

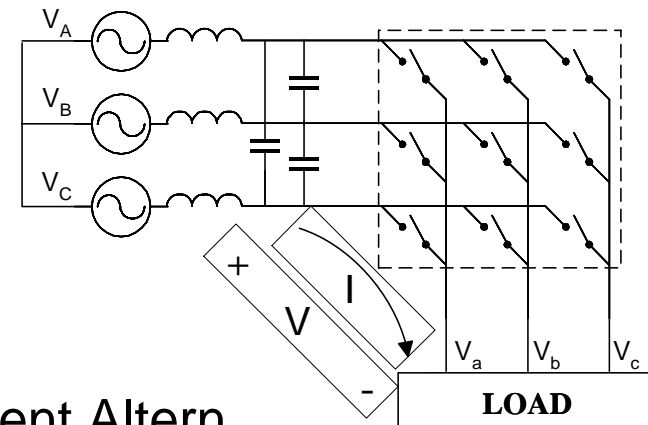
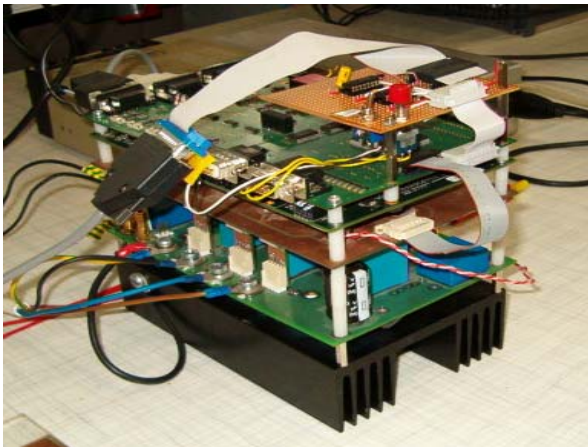
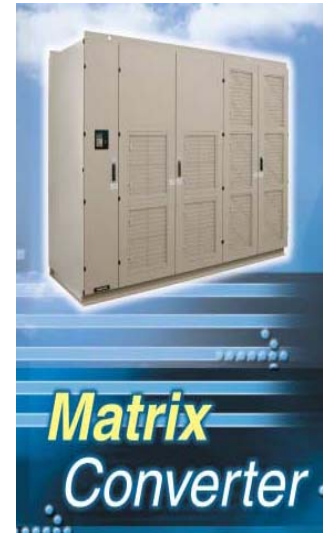


Notes on Matrix Converters

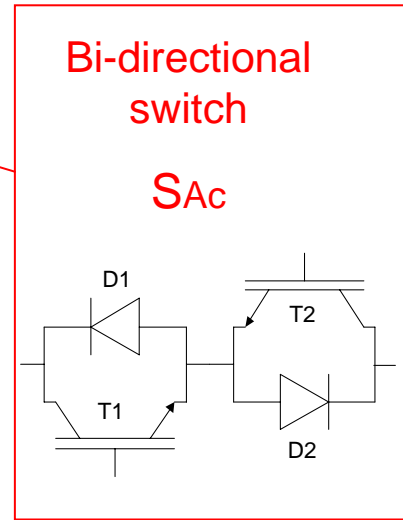

CECA – Convertidors Estàtics de Corrent Altern

Dr. Antoni Arias

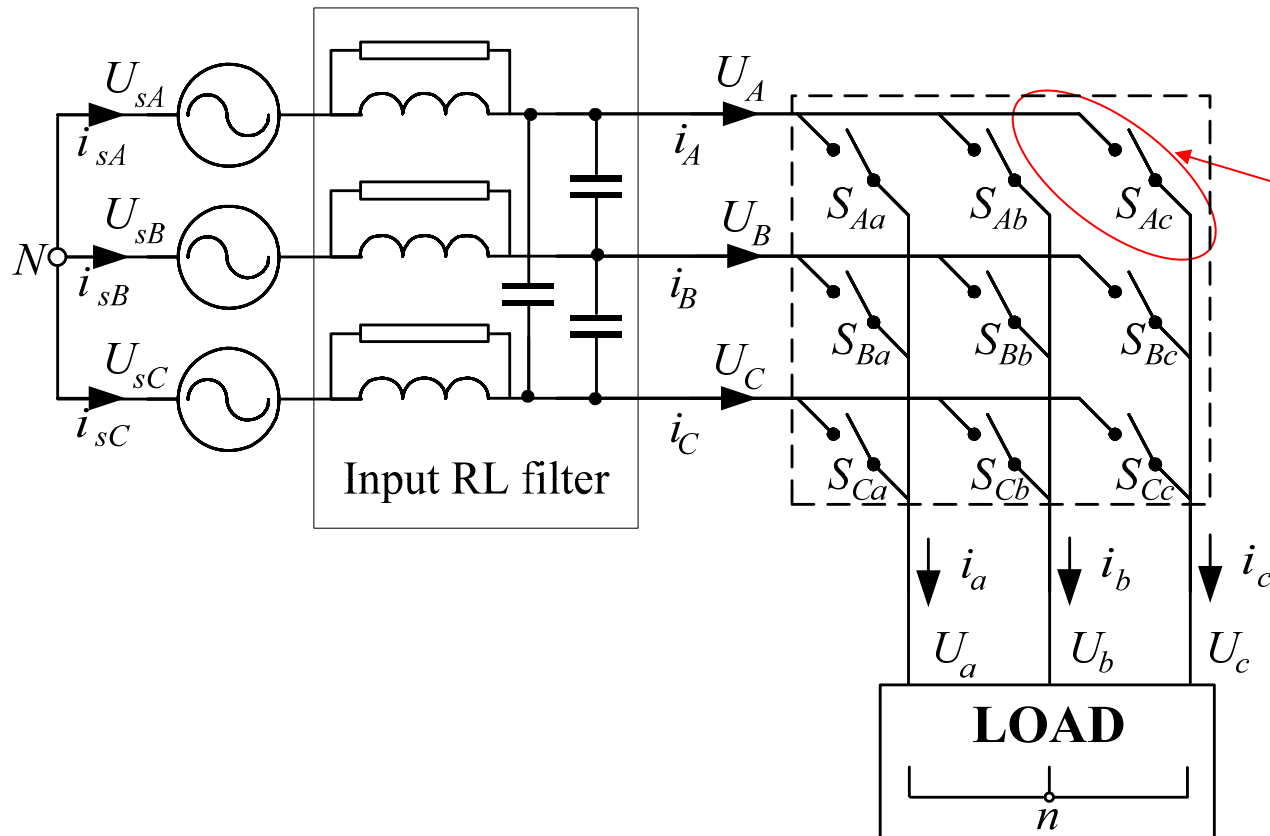


- AC / AC direct electrical power conversion
- $M \times N$, inputs & outputs. Figure corresponds to the 3×3
- Variable frequency and variable voltage

- Switching function: $S_{io}(t) = \begin{cases} 1, & \text{open} \\ 0, & \text{closed} \end{cases}$

$$i = \{A, B, C\}$$

$$o = \{a, b, c\}$$

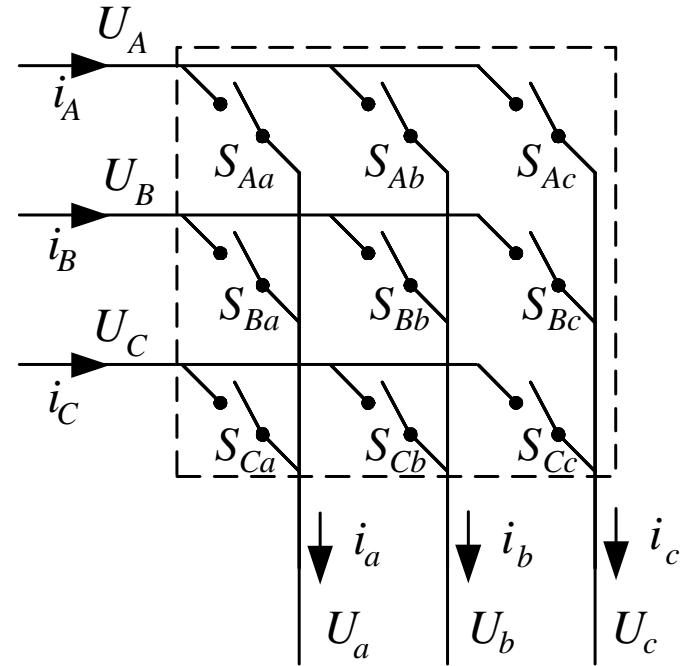- Transfer Matrix:
$$[T] = \begin{bmatrix} S_{Aa}(t) & S_{Ba}(t) & S_{Ca}(t) \\ S_{Ab}(t) & S_{Bb}(t) & S_{Cb}(t) \\ S_{Ac}(t) & S_{Bc}(t) & S_{Cc}(t) \end{bmatrix}$$



- There are 2^9 (512) possible combinations
- Each output phase can be connected to any input phase
- There are several constraints:
 - Avoid line to line input short circuit
 - Avoid open circuits with inductive currents

$$S_{Ao}(t) + S_{Bo}(t) + S_{Co}(t) = 1$$


$$[U_{oN}(t)] = \begin{bmatrix} U_{aN}(t) \\ U_{bN}(t) \\ U_{cN}(t) \end{bmatrix}$$

$$[U_{iN}(t)] = \begin{bmatrix} U_{AN}(t) \\ U_{BN}(t) \\ U_{CN}(t) \end{bmatrix}$$

$$[i_o(t)] = \begin{bmatrix} i_a(t) \\ i_b(t) \\ i_c(t) \end{bmatrix}$$

$$[i_i(t)] = \begin{bmatrix} i_A(t) \\ i_B(t) \\ i_C(t) \end{bmatrix}$$
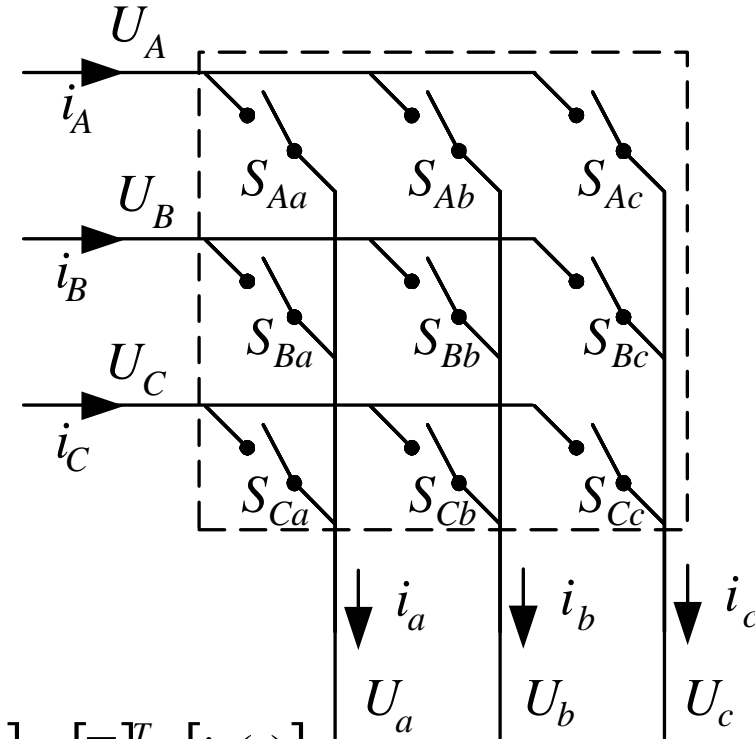
$$i = \{A, B, C\} \quad o = \{a, b, c\}$$



$$[U_{oN}(t)] = [T] \cdot [U_{iN}(t)]$$

$$[i_i(t)] = [T]^T \cdot [i_o(t)]$$

$$\begin{bmatrix} U_{aN}(t) \\ U_{bN}(t) \\ U_{cN}(t) \end{bmatrix} = \begin{bmatrix} S_{Aa}(t) & S_{Ba}(t) & S_{Ca}(t) \\ S_{Ab}(t) & S_{Bb}(t) & S_{Cb}(t) \\ S_{Ac}(t) & S_{Bc}(t) & S_{Cc}(t) \end{bmatrix} \cdot \begin{bmatrix} U_{AN}(t) \\ U_{BN}(t) \\ U_{CN}(t) \end{bmatrix}$$

$$\begin{bmatrix} i_A(t) \\ i_B(t) \\ i_C(t) \end{bmatrix} = \begin{bmatrix} S_{Aa}(t) & S_{Ab}(t) & S_{Ac}(t) \\ S_{Ba}(t) & S_{Bb}(t) & S_{Bc}(t) \\ S_{Ca}(t) & S_{Cb}(t) & S_{Cc}(t) \end{bmatrix} \cdot \begin{bmatrix} i_a(t) \\ i_b(t) \\ i_c(t) \end{bmatrix}$$

- Direct AC / AC Conversion. No DC Link: all silicon solution
 - Less bulky (compact motor drives)
 - Safer (hostile environments: aircraft, submarine...)
- Bidirectional power flow
- 4 quadrant converter
- Sinusoidal input and output currents waveforms
- No restriction on input and output frequency within limits imposed by switching frequency
- Output voltage limited to 86.6% ($\cos 30^\circ$) of input voltage
- 9 bidirectional switches. (18 IGBT + 18 Diodes)


- Industrial Products:


- Yaskawa FSDrive-MX1S.

- Launched in 2004
- World's first matrix converter Drive
- Super energy –saving medium-voltage Matrix Converter with Power regeneration
- 3kV 200 to 3000kVA
- 6kV 400 to 6000kVA
- Applications:
 - Wind/Water Force Machines (blowers, boilers, incinerators), pumps, and general Industrial Machines.


- Applications:

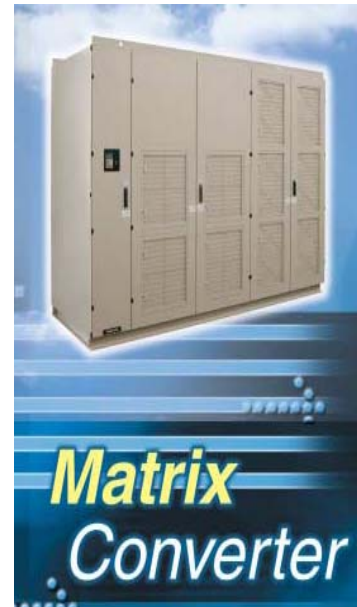- Compact or Integrated Motor Drives
- Motor Drives for hostile environments (aircrafts, submarines)
- AC/AC Power Conversions: wind energy, variable speed drives...




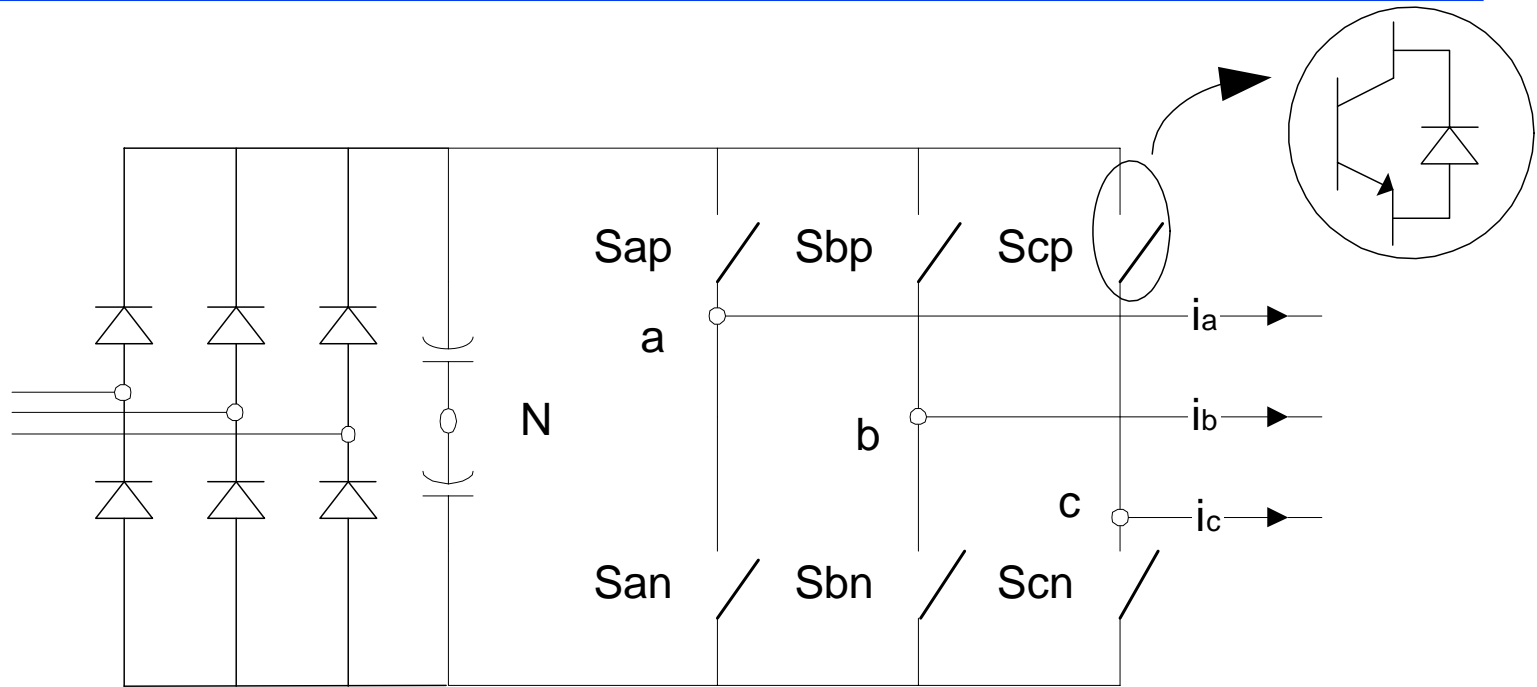

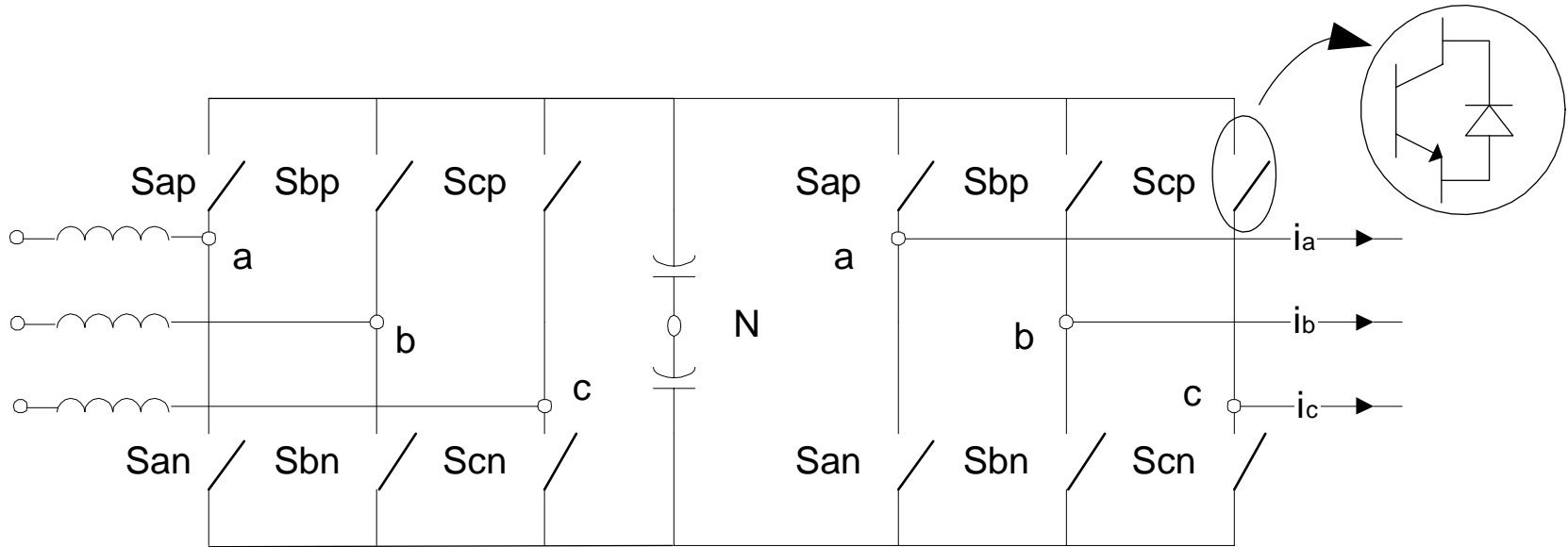
- Industry “workhorse” from less than kW to MW
- Unidirectional power flow
- 2 quadrant
 - When the current changes its sign, the power must be burn in the DC link
- DC link capacitor (30% -50% of the power circuit volume)
- Input currents very poor. (awful THD)



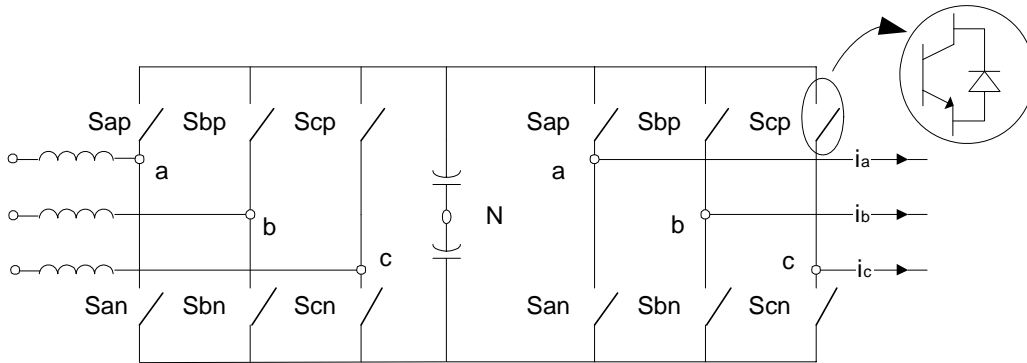- Bi directional power flow
- 4 quadrant
- DC link capacitor and input inductors
- Sinusoidal input currents. Input Power Factor 1
- *Matrix Converter real alternative*




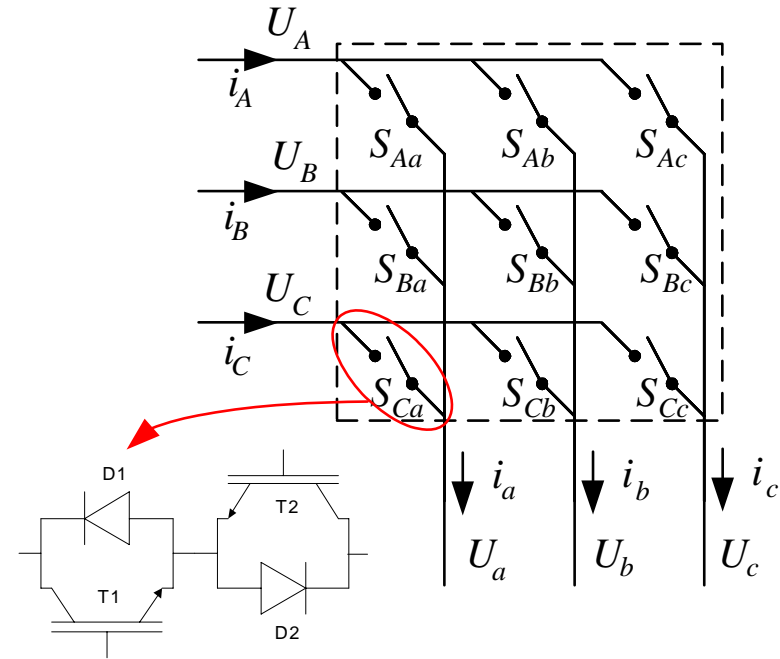- 12 IGBTs + 12 Diodes
- 1 large electrolytic capacitor (DC link)
- Input filter (1st order)
 - 3 large inductors




- 18 IGBTs + 18 Diodes
- Input filter (2nd order)
 - 3 inductors
 - 3 capacitors
- *Clamp circuit*

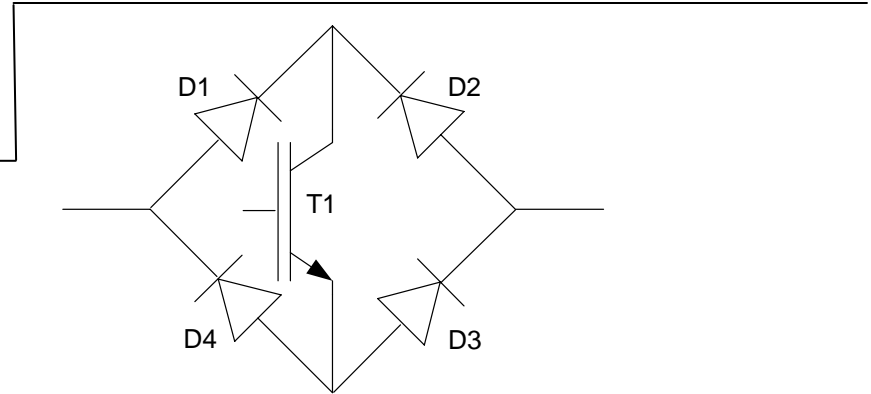- Must be able to conduct positive and negative current and block positive and negative voltage




- Diode embedded switch
 - Switch: 1 IGBT + 4 diodes
 - Conducting losses: 2 diodes +1 IGBT

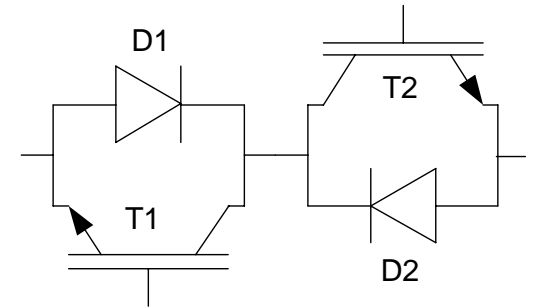
- Back to back switch with common collector
 - Switch: 2 IGBT + 2 diodes
 - Diode required for reverse blocking capability
 - Conducting losses: 1 diode +1 IGBT



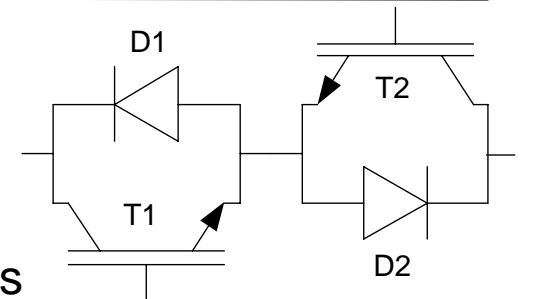- Back to back switch with common emitter
 - Switch: 2 IGBT + 2 diodes
 - Diode required for reverse blocking capability
 - Conducting losses: 1 diode +1 IGBT
 - No need of isolation between both gate power supplies



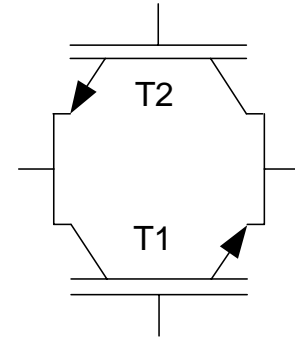
- Reverse Blocking IGBT, RBIGBT
 - Two reverse blocking IGBTs
 - Lower conducting losses: one switching device
 - *Still under research*
 - *Switch control will remain the same*



SUMMARY

	<i>IGBTs</i>	Diodes	Isolated Power Supplies	Conducting Devices
Diode bridge	9	36	9	3
Common Emitter	18	18	9	2
Common Collector	18	18	6	2

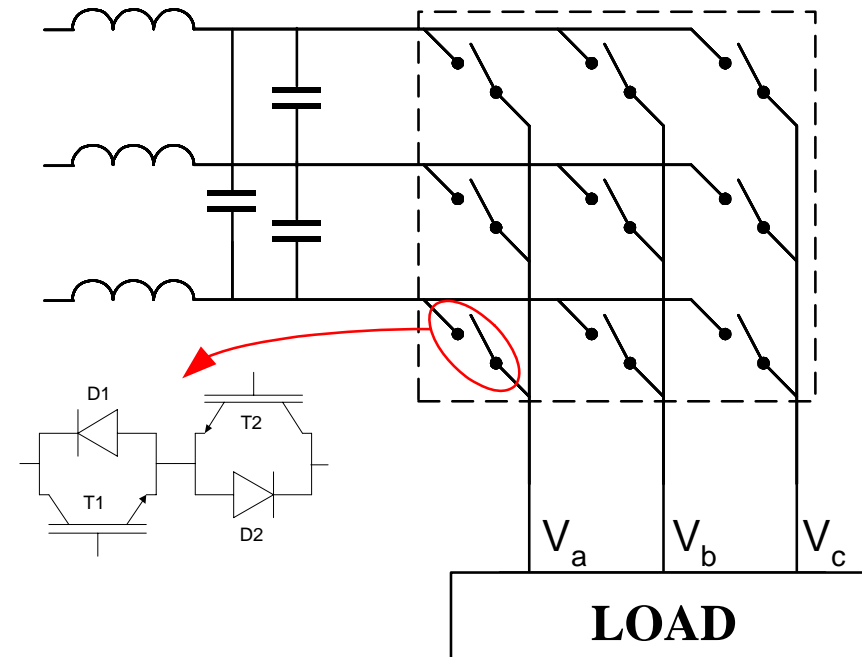- Dynex 200 (A) Bi directional Module
 - From standard one leg conventional VSI
 - 9 for a 3x3MC
 - Large Converters > 200 (A)
 - Common collector



...announced the release of two bi-directional IGBT modules for use in matrix converter power stages...



...Dynex Semiconductor is working closely with researchers at Nottingham University. Through this collaboration and in response to commercial requirements, Dynex has created the DIM400PBM17-A000 for use in a 60Hz to 400Hz fixed frequency converter and the GP200MBS12 for use in a high efficiency brushless dc motor drive.

The DIM400PBM17-A000 module is a 400A 1700V bi-directional switch mounted on a 140mm x 73mm metal matrix baseplate. Long-term reliability and enhanced thermal performance are achieved through the use of aluminium nitride substrates mounted on a metal matrix compound baseplate. The package has a 6 kV isolation rating...

...The DIM200MBS12-A000 module is a 200A 1200V bi-directional switch mounted on a 106mm x 62mm copper baseplate. The package has a 4 kV isolation rating...

<http://www.dynexsemi.com/corporate/news/items/20020514-prod-b.htm>

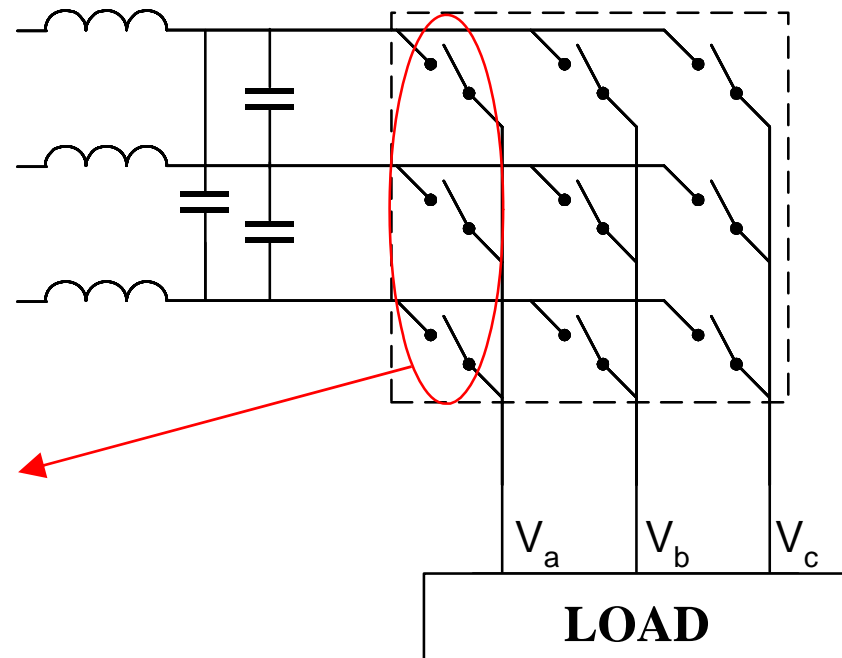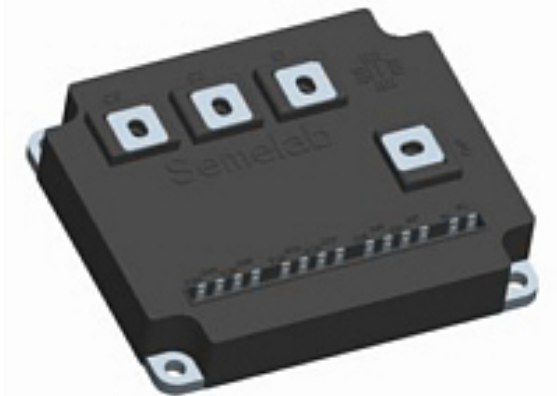
- SEMELAB 200 (A) Bi directional Module
 - 3 for a 3x3MC
 - Large Converters



A Matrix Converter IGBT Bi-Directional switching module



A 360kVA (600V max line-line at up to 300A) matrix converter module designed by Semelab.

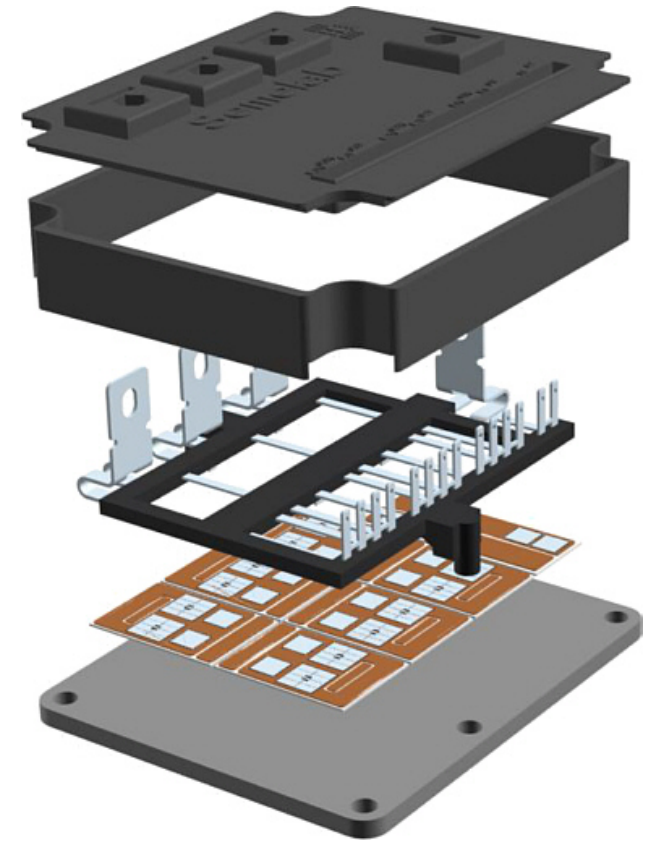
- IGBT Packaging Available in 300V to 1800V
- Aerospace
- Customised to fit your needs.
- Good CTE match, from Silicon to the metal matrix base plate.
- Excellent reliability module, temp cycling, humidity tested, elevated pressure.
- Low power losses.
- Plastic package / Hermetic packaging
- Power connection,
- Mounting holes
- Void free die attach, X-ray capability.




<http://www.semelab.co.uk/power/>

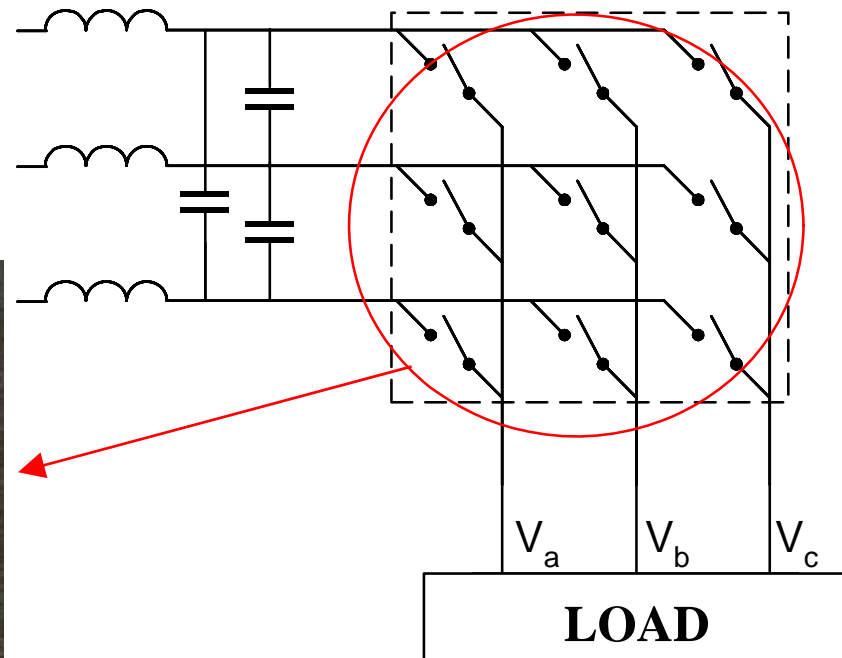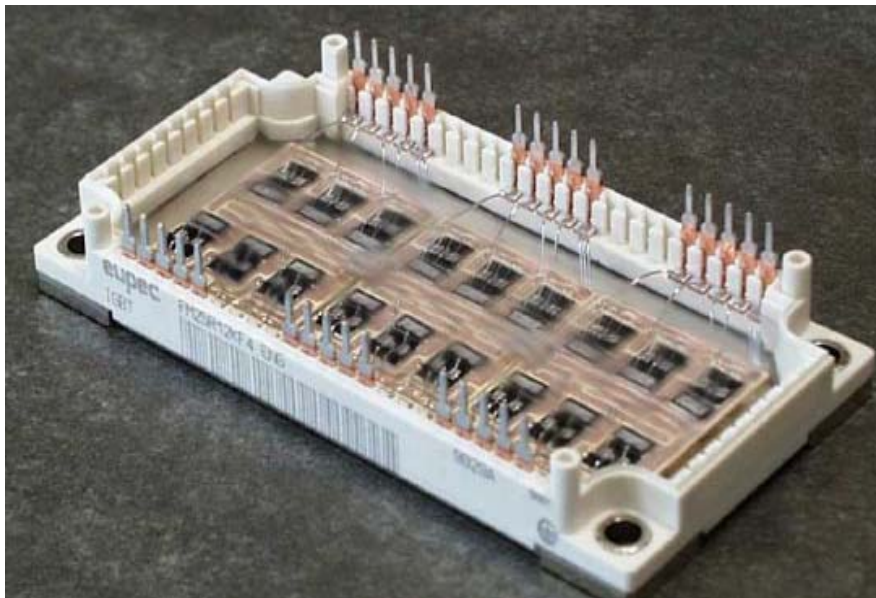- EUPEC 35A Matrix Converter Module
 - 1 for a 3x3MC
 - Small Powers Converters. 7.5 kW



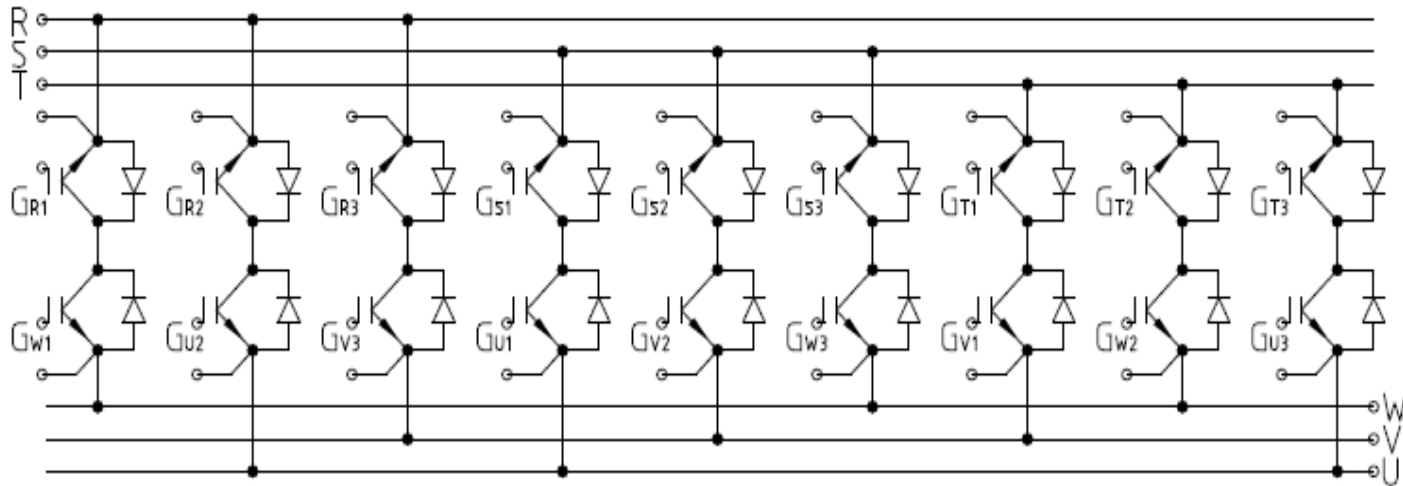

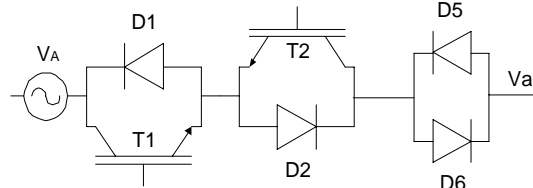- Current commutation
 - Needs the sign of the output current per phase
 - Add two anti parallel diodes and measure its voltage drops





- Measure the device voltage drops




- Most widely used

- Voltage commutation
 - Needs the input voltage values per phase

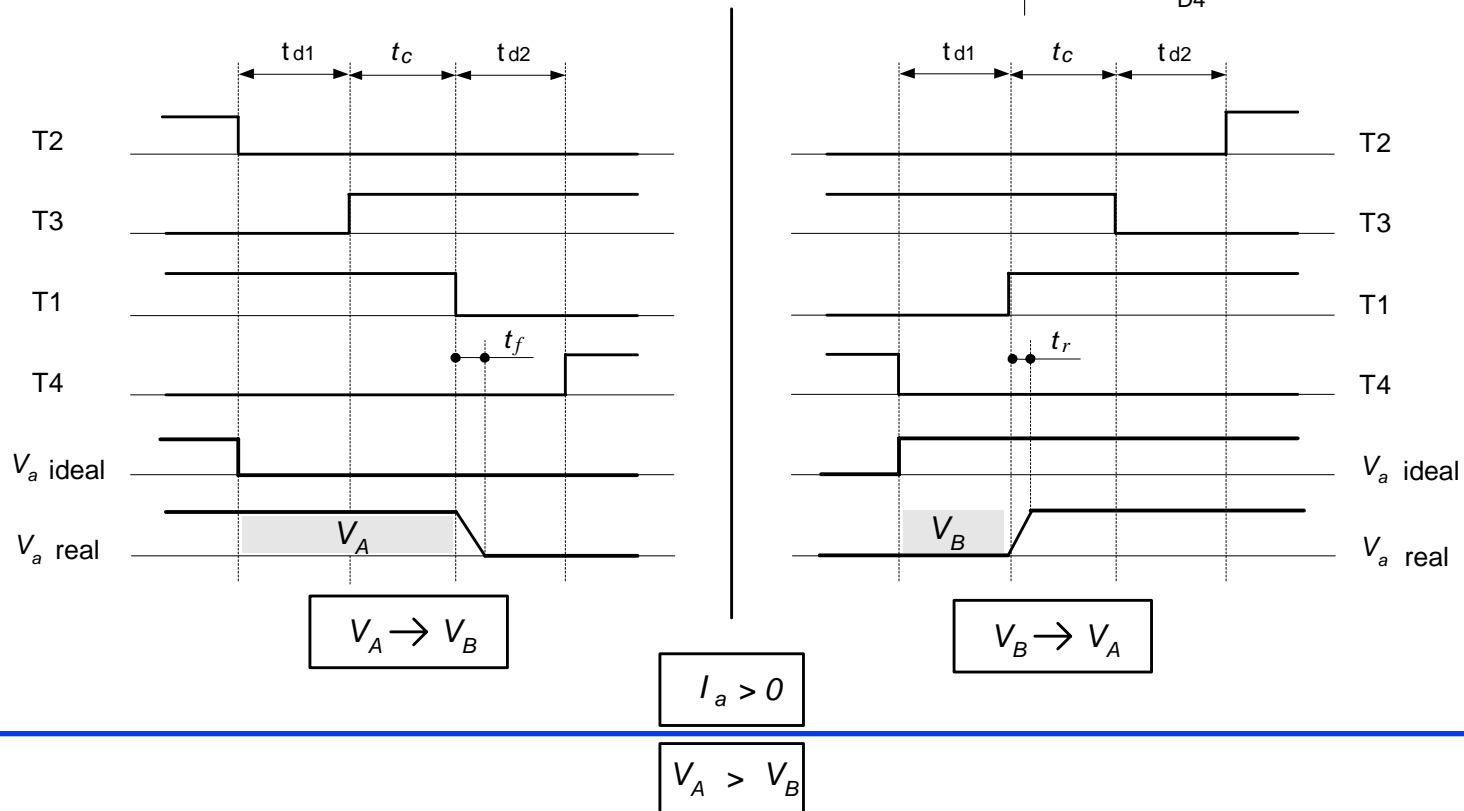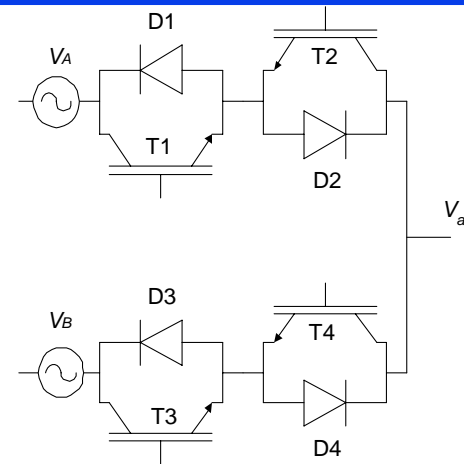- No short circuits at the input
- No open circuit at the output (inductive loads)




4 Step Current Commutation

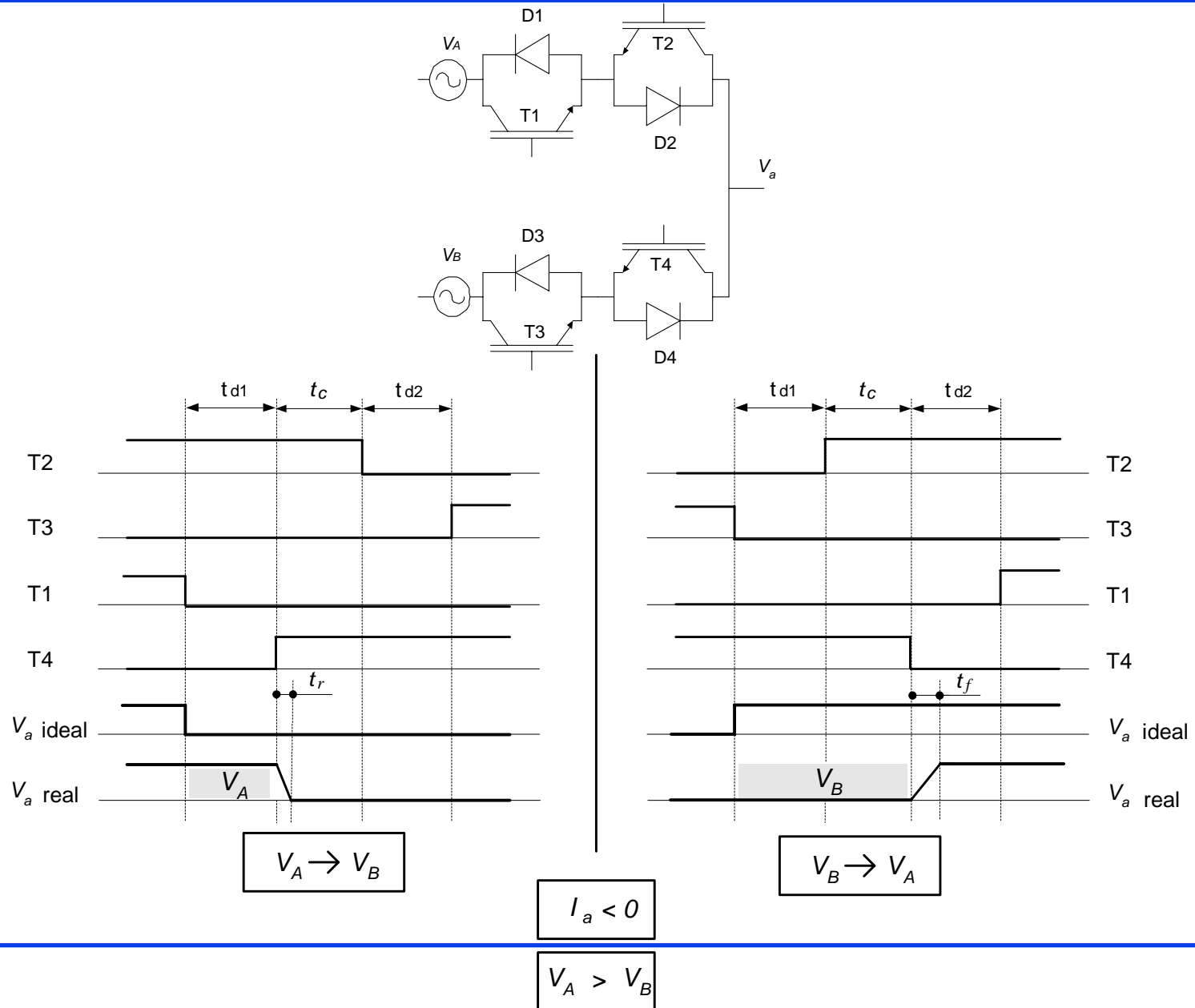


Matrix Converter	
EUPEC FM35R12KE3ENG module	
Switching device	1200V, 35 A, IGBT
$t_{d1} / t_c / t_{d2}$	1 / 0.2 / 0.5 μ s
t_f / t_r	65-90 ns / 30-45 ns
Power	7.5 kW
<i>AC Input voltage</i>	<i>3 x 415V</i>
<i>Input filter (L/C) values</i>	<i>1mH / 1.5μF</i>

- 2nd Order Input L-C filter
 - Typical cut off frequency 1-3 kHz
 - between the fundamental 0-100Hz
 - and the PWM frequency 10-20 kHz
 - R in parallel with L in order to have an adequate damping
 - L impedance at 100Hz should be negligible
 - $2 \cdot \pi \cdot f \cdot L = 2 \cdot 3.14 \cdot 100 \cdot 10^{-3} = 0.628$ ohms


Matrix Converter	
EUPEC FM35R12KE3ENG module	
Switching device	1200V, 35 A, IGBT
Power	7.5 kW
AC Input voltage	3 x 415V
Input filter (L/C) values	1mH / 1.5μF

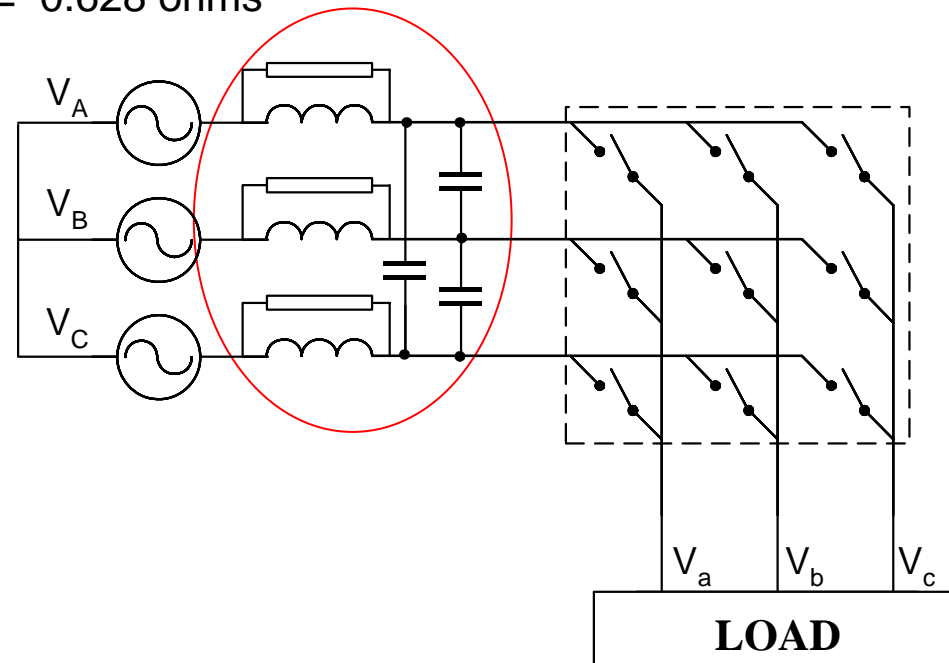

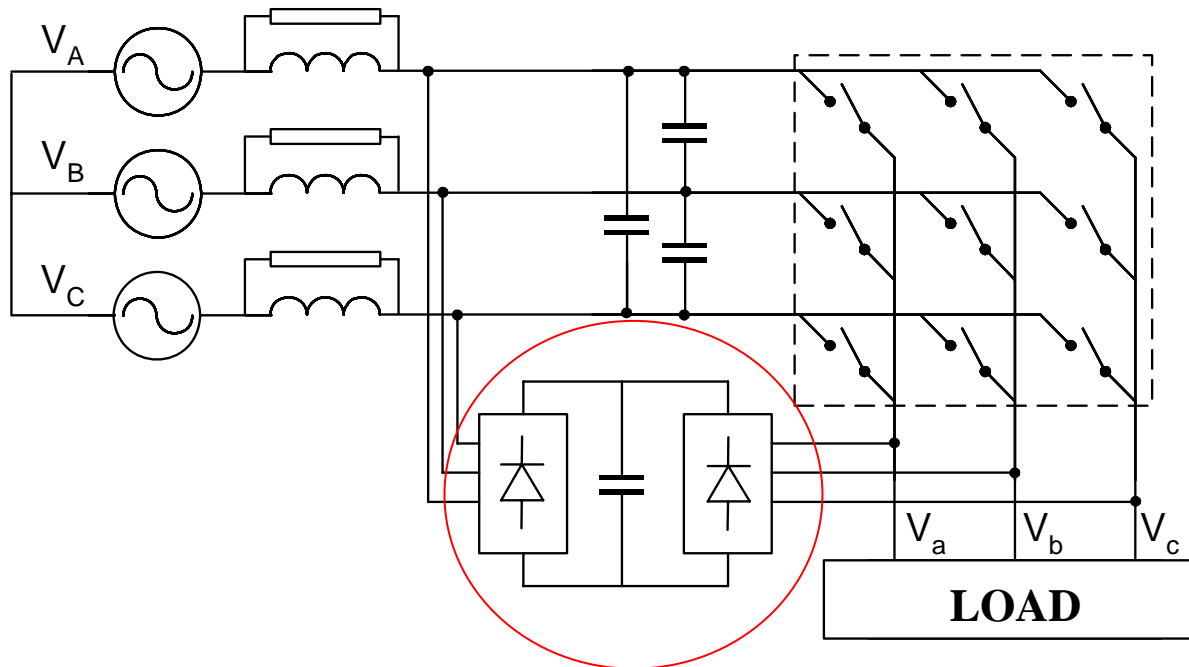- Diode bridge like a standard rectifier
- Protection against
 - open circuits with inductive currents
 - over voltage caused by transients in power up and voltage sags




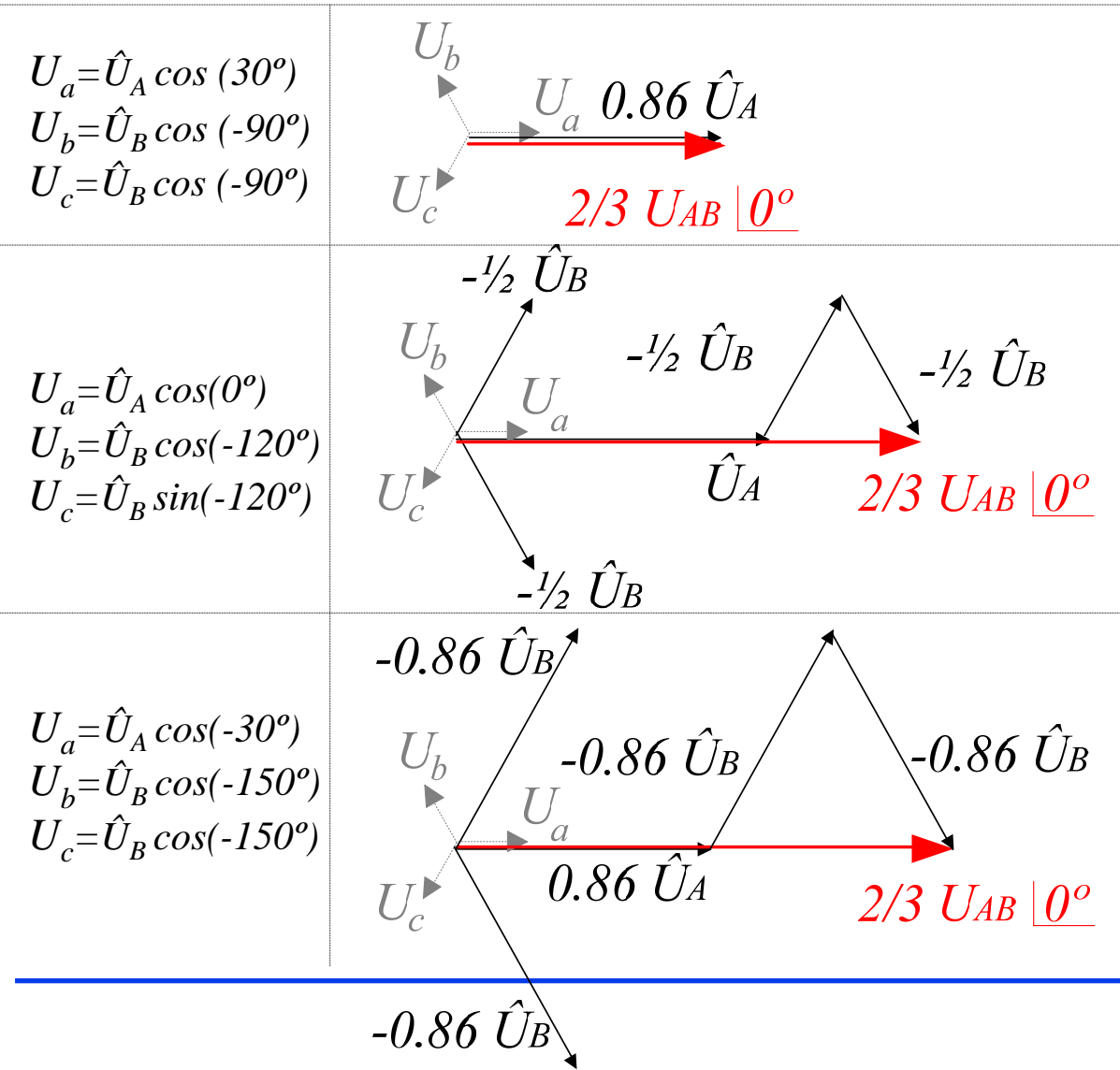
- Space Vector Concept: $\vec{U}_o(t) = \frac{2}{3} (U_a(t) + U_b(t) \cdot e^{j2\pi/3} + U_c(t) \cdot e^{j4\pi/3})$






State +1
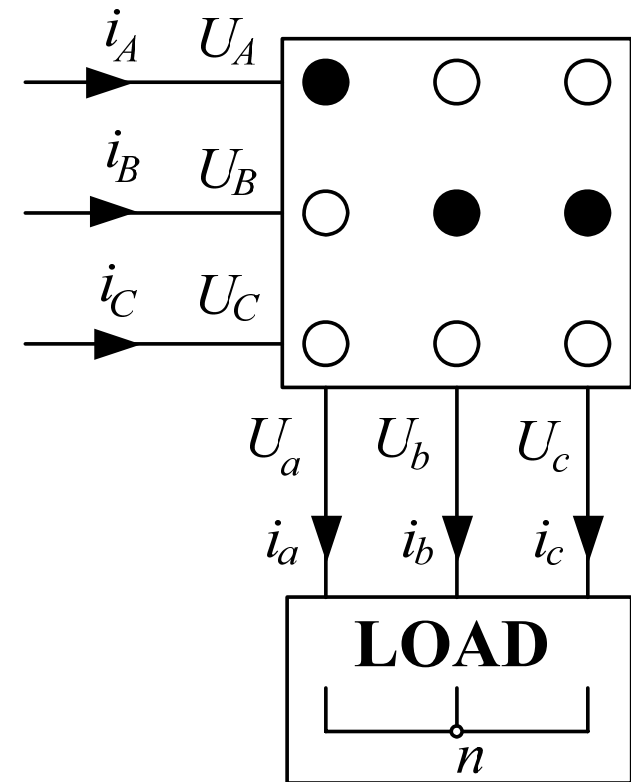
$$U_a = U_A \quad U_b = U_B \quad U_c = U_B$$




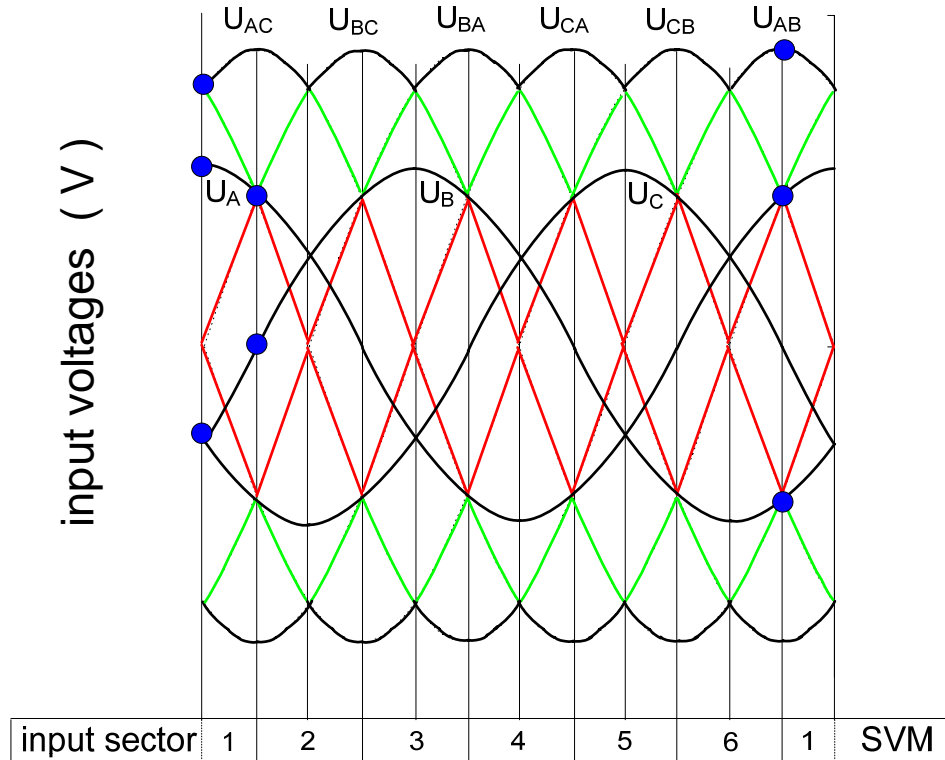


- Variable amplitude
- Same angle

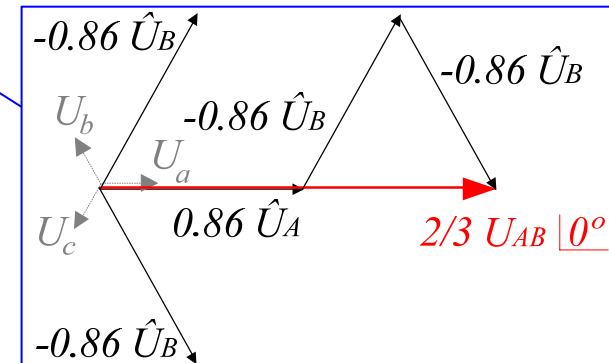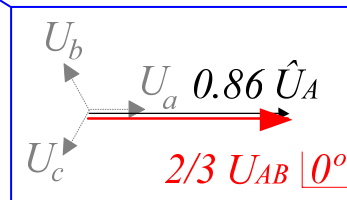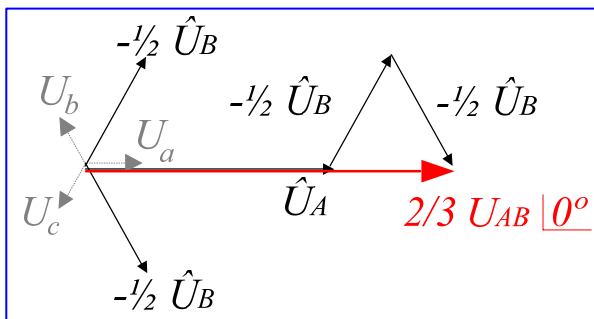

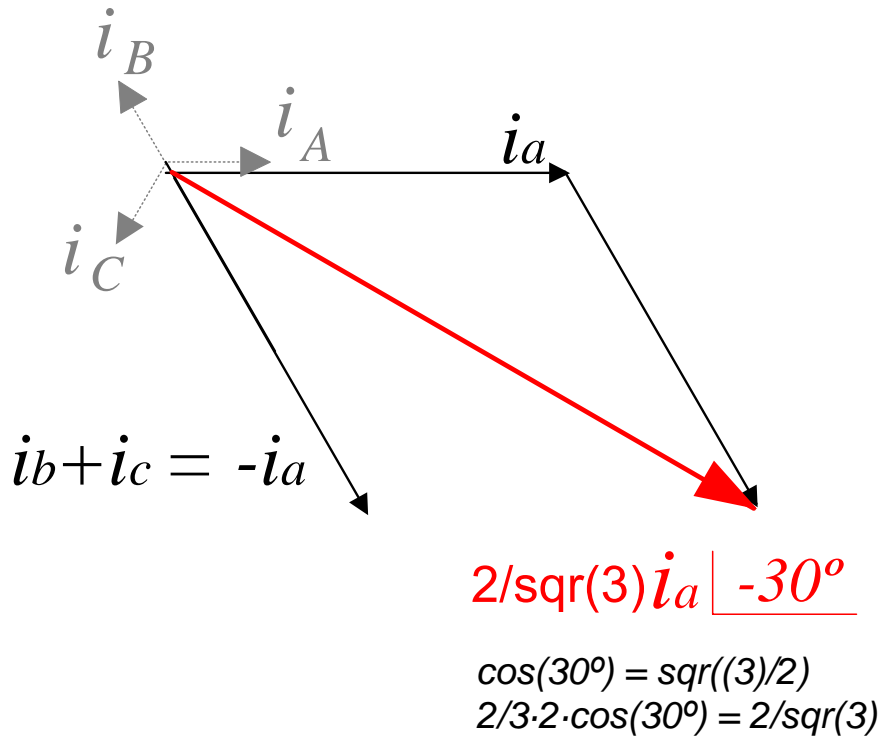- Space Vector Concept: $\vec{i}_i(t) = \frac{2}{3} (i_A(t) + i_B(t) \cdot e^{j2\pi/3} + i_C(t) \cdot e^{j4\pi/3})$



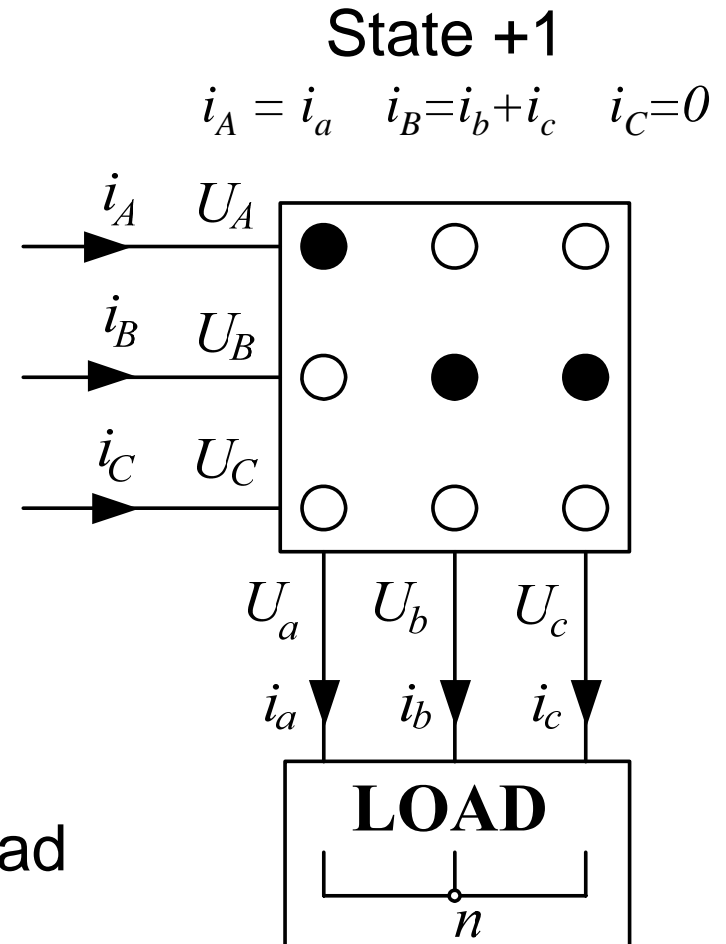
- Amplitude dependant on the load
- Same angle



	$a b c$	$ \vec{V}_o $	α_o	$ \vec{i}_i $	β_i
+1	A B B	$2/3U_{AB}$	0	$2/\text{sqr}(3) i_a$	$11\pi/6$
+2	B C C	$2/3U_{BC}$	0	$2/\text{sqr}(3) i_a$	$\pi/2$
+3	C A A	$2/3U_{CA}$	0	$2/\text{sqr}(3) i_a$	$7\pi/6$
+4	B A B	$2/3U_{AB}$	$2\pi/3$	$2/\text{sqr}(3) i_b$	$11\pi/6$
+5	C B C	$2/3U_{BC}$	$2\pi/3$	$2/\text{sqr}(3) i_b$	$\pi/2$
+6	A C A	$2/3U_{CA}$	$2\pi/3$	$2/\text{sqr}(3) i_b$	$7\pi/6$
+7	B B A	$2/3U_{AB}$	$4\pi/3$	$2/\text{sqr}(3) i_c$	$11\pi/6$
+8	C C B	$2/3U_{BC}$	$4\pi/3$	$2/\text{sqr}(3) i_c$	$\pi/2$
+9	A A C	$2/3U_{CA}$	$4\pi/3$	$2/\text{sqr}(3) i_c$	$7\pi/6$
+R1	A B C	$\hat{U}i$	$[\hat{U}i]$	i_{oMAX}	$[i_{oMAX}]$
+R2	C A B	$\hat{U}i$	$[\hat{U}i+2\pi/3]$	i_{oMAX}	$[i_{oMAX}+2\pi/3]$
+R3	B C A	$\hat{U}i$	$[\hat{U}i+4\pi/3]$	i_{oMAX}	$[i_{oMAX}+4\pi/3]$
0_A	A A A	0	0
0_B	B B B	0	0
0_C	C C C	0	0


	$a b c$	$ \vec{V}_o $	α_o	$ \vec{i}_i $	β_i
-1	B A A	$-2/3U_{AB}$	0	$-2/\text{sqr}(3) i_a$	$11\pi/6$
-2	C B B	$-2/3U_{BC}$	0	$-2/\text{sqr}(3) i_a$	$\pi/2$
-3	A C C	$-2/3U_{CA}$	0	$-2/\text{sqr}(3) i_a$	$7\pi/6$
-4	A B A	$-2/3U_{AB}$	$2\pi/3$	$-2/\text{sqr}(3) i_b$	$11\pi/6$
-5	B C B	$-2/3U_{BC}$	$2\pi/3$	$-2/\text{sqr}(3) i_b$	$\pi/2$
-6	C A C	$-2/3U_{CA}$	$2\pi/3$	$-2/\text{sqr}(3) i_b$	$7\pi/6$
-7	A A B	$-2/3U_{AB}$	$4\pi/3$	$-2/\text{sqr}(3) i_c$	$11\pi/6$
-8	B B C	$-2/3U_{BC}$	$4\pi/3$	$-2/\text{sqr}(3) i_c$	$\pi/2$
-9	C C A	$-2/3U_{CA}$	$4\pi/3$	$-2/\text{sqr}(3) i_c$	$7\pi/6$
-R1	A C B	$\hat{U}i$	$[-\hat{U}i]$	i_{oMAX}	$[-i_{oMAX}]$
-R2	B A C	$\hat{U}i$	$[-\hat{U}i+2\pi/3]$	i_{oMAX}	$[-i_{oMAX}+2\pi/3]$
-R3	C B A	$\hat{U}i$	$[-\hat{U}i+4\pi/3]$	i_{oMAX}	$[-i_{oMAX}+4\pi/3]$

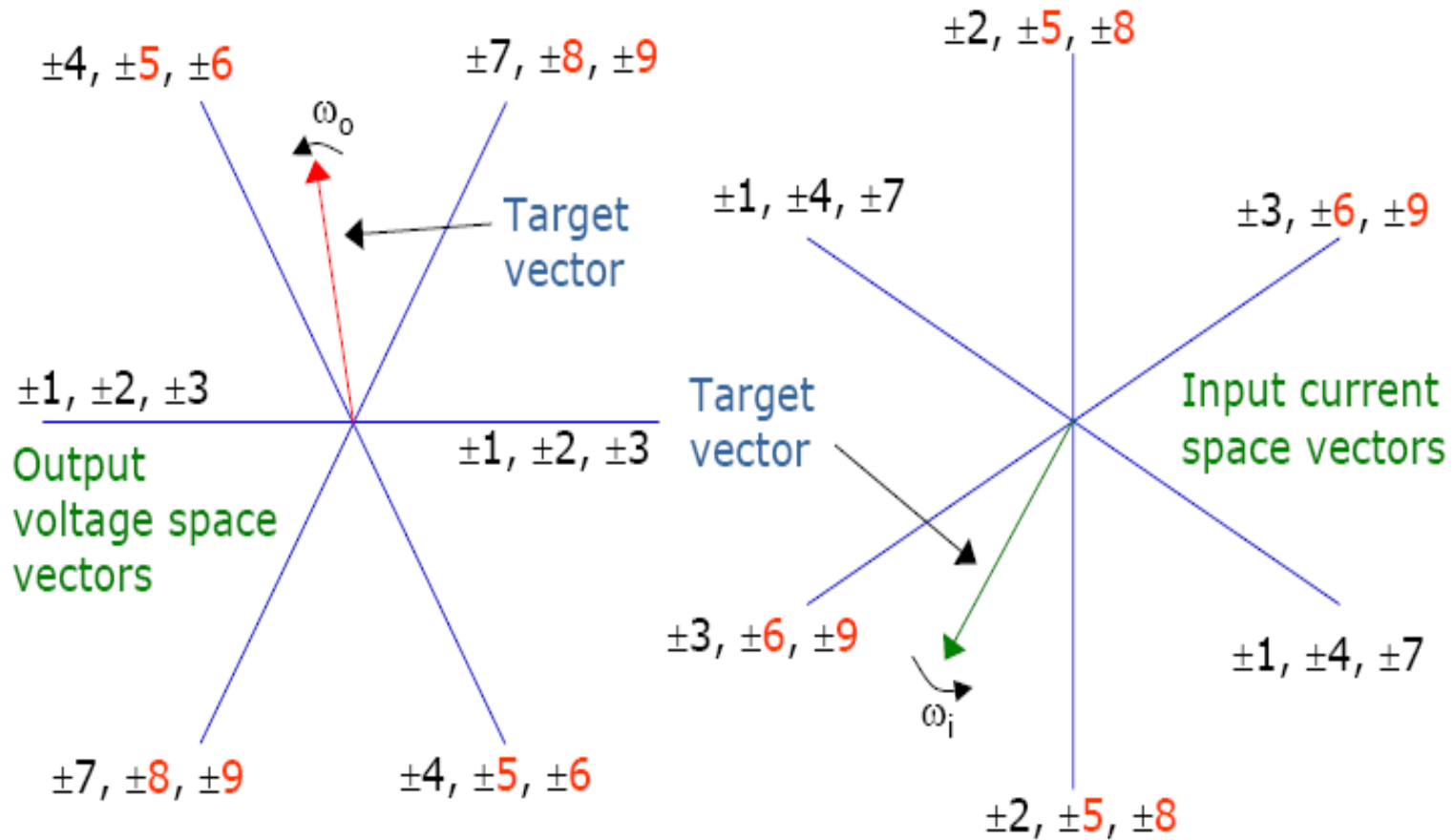27 vectors: 18 constant in direction + 3 nulls + 6 rotating




- PWM Modulation technique is applied in order to:
 - follow a reference at the output, which on average will be a sinusoidal
 - get sinusoidal input currents on phase with the input voltage (power factor 1)
- Several modulation techniques:
 - Venturini, Scalar...
- Direct Space Vector Modulation
- Indirect Space Vector Modulation
 - Based on the Space Vector Modulation for Standard PWM Inverters
 - There are two reference vectors:
 - Input current
 - Output voltage

Rectification stage

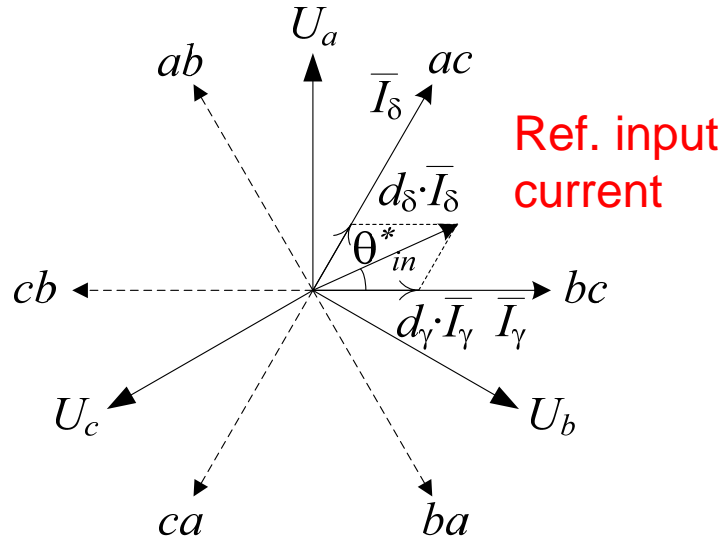

Inversion stage

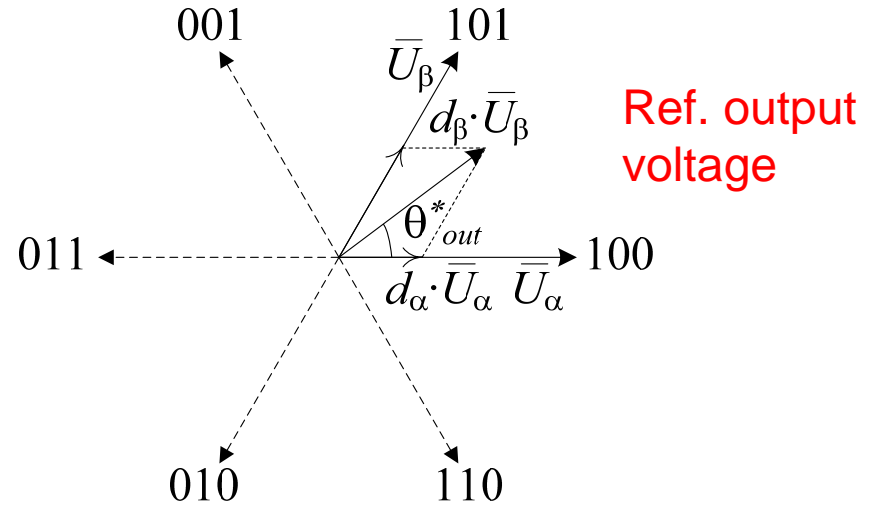

$$d_\gamma = m_I \cdot \sin\left(\frac{\pi}{3} - \theta_{in}^*\right) \quad d_\delta = m_I \cdot \sin(\theta_{in}^*) \quad d_\alpha = m_U \cdot \sin\left(\frac{\pi}{3} - \theta_{out}^*\right) \quad d_\beta = m_U \cdot \sin(\theta_{out}^*)$$


- To obtain a correct balance of the input currents and the output voltages, the modulation pattern should be a combination of all 4 duty-cycles


$$d_{\alpha\gamma} = d_\alpha \cdot d_\gamma \quad d_{\alpha\delta} = d_\alpha \cdot d_\delta \quad d_{\beta\delta} = d_\beta \cdot d_\delta \quad d_{\beta\gamma} = d_\beta \cdot d_\gamma$$


- And the zero vector is calculated as follows

$$d_0 = 1 - (d_{\alpha\gamma} + d_{\alpha\delta} + d_{\beta\delta} + d_{\beta\gamma})$$

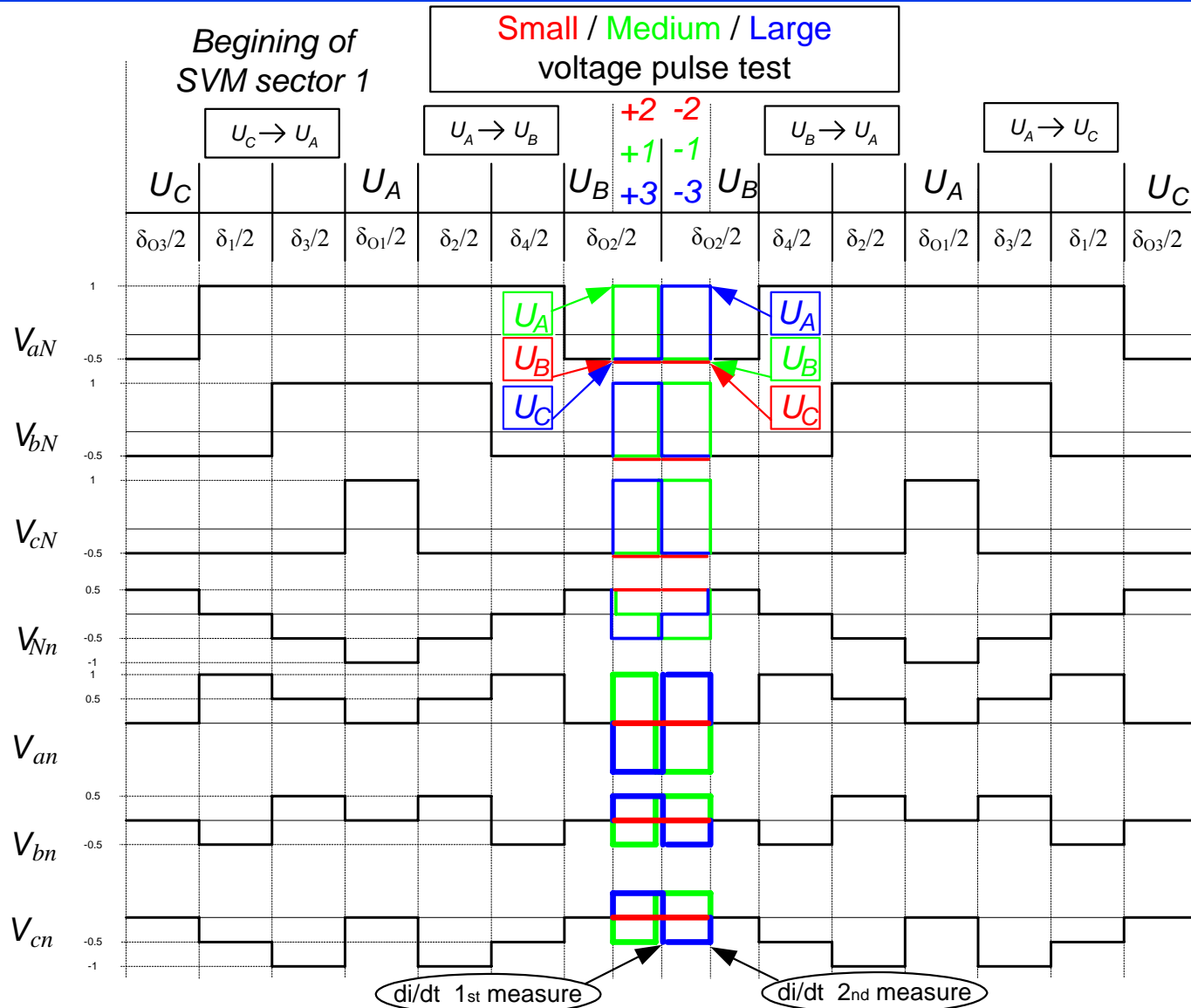- The typical modulation pattern is as shown in next slide



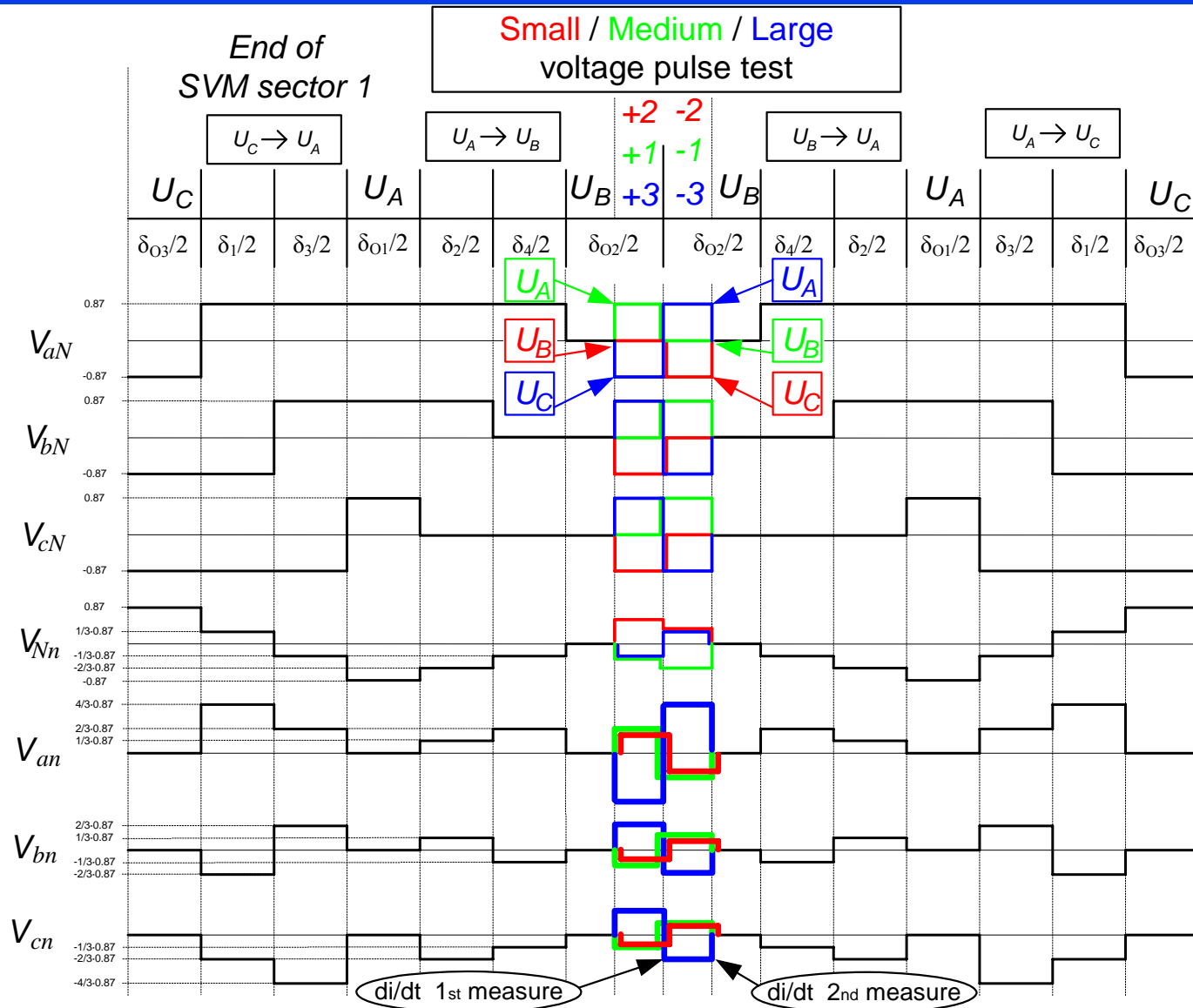


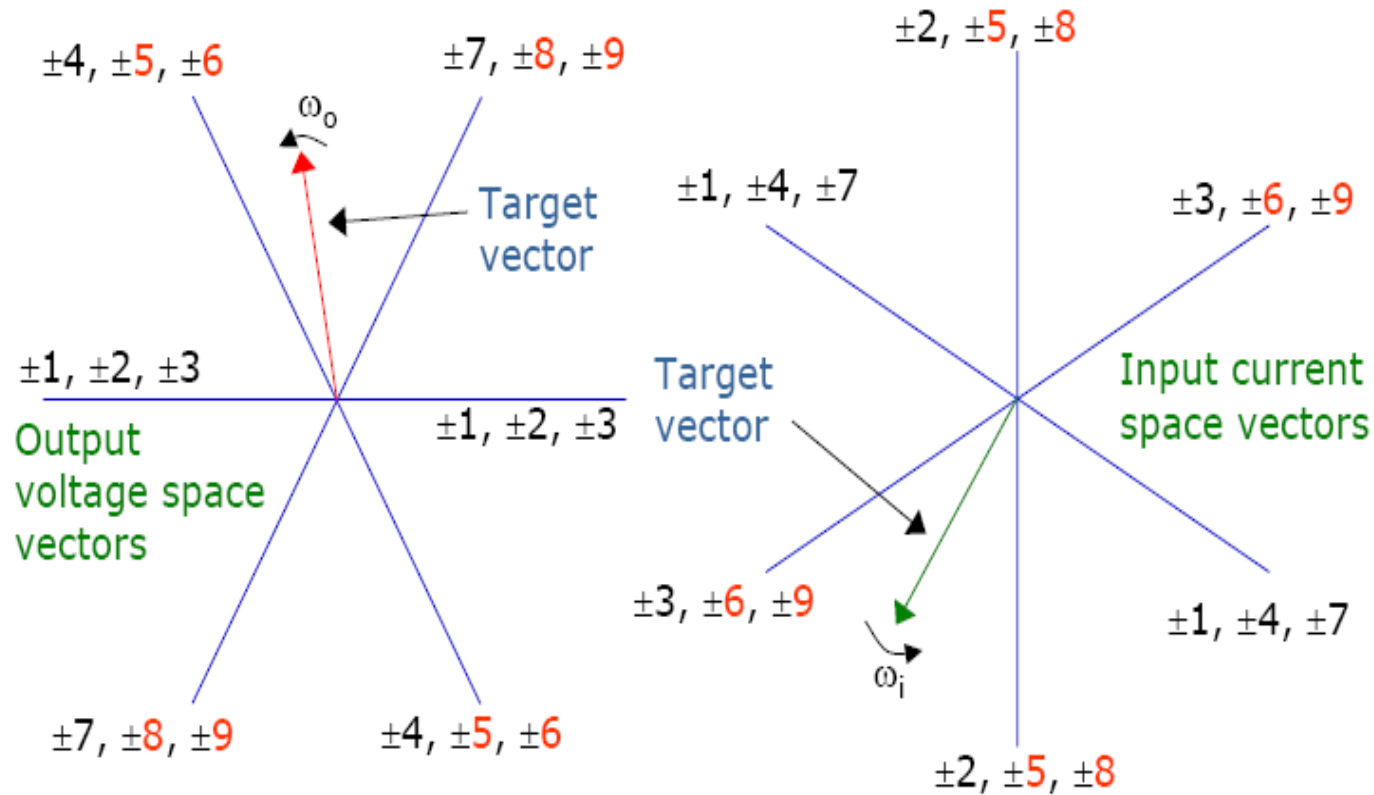



- In such case the four active states used would be:
 - 5,6,8 and 9
 - There will always be four vectors: 2 for the inversion stage and 2 for the rectifier stage.

Matrix Converter linearization


- General scheme

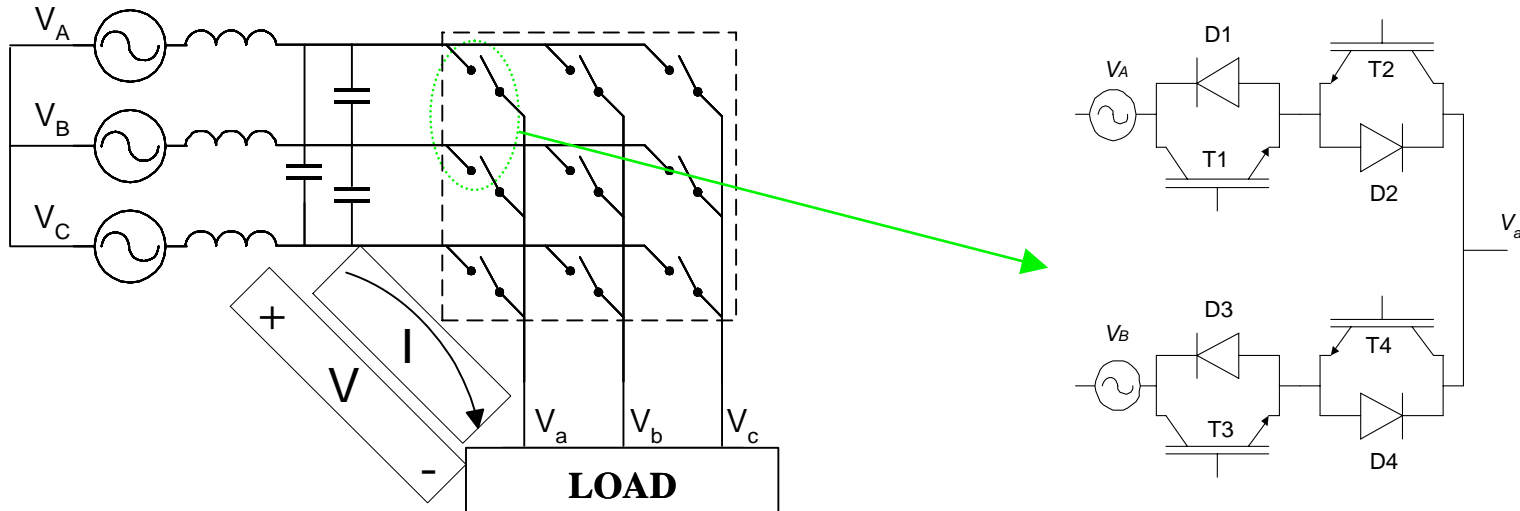


- Voltage Drop effect

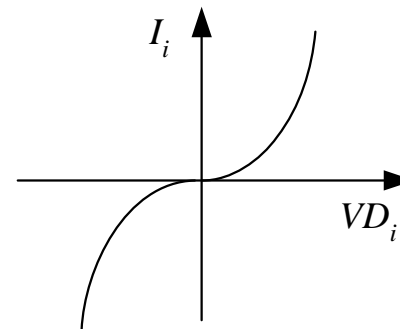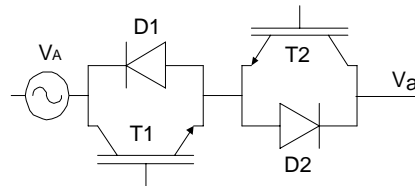

Matrix Converter linearization

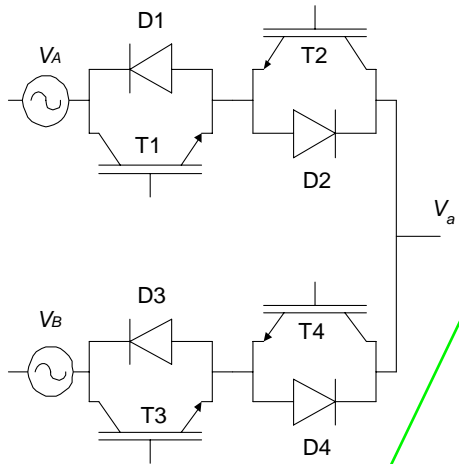

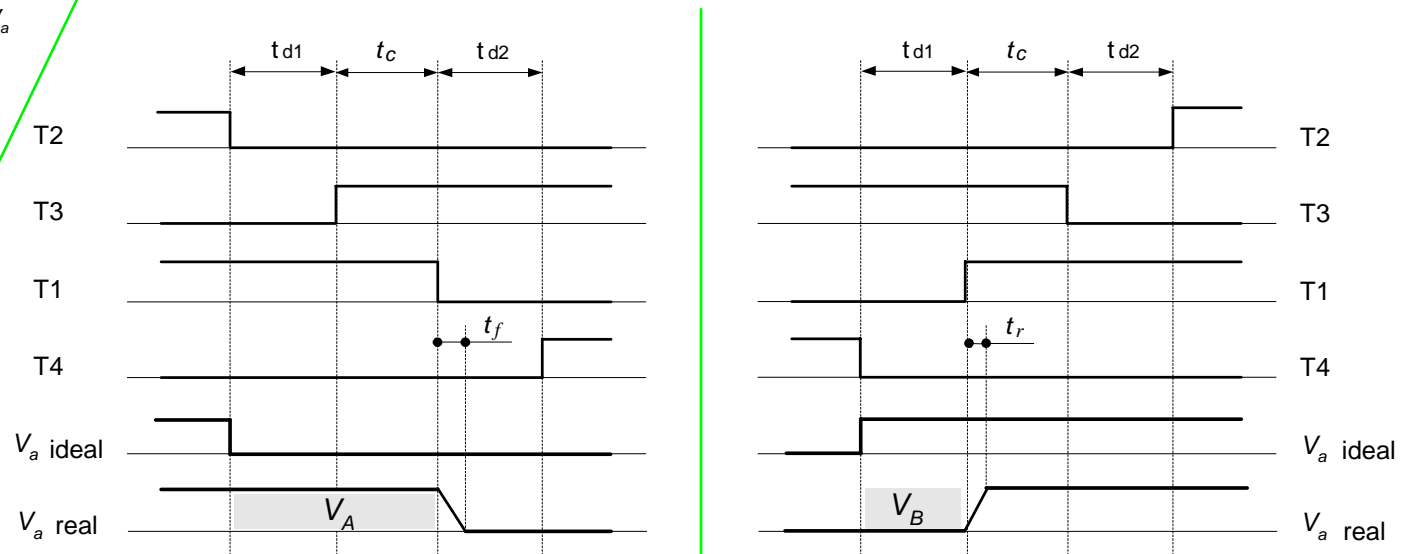- Four step commutation
- $(t_{d1} + t_c + t_{d2} = 1\mu\text{s} + 0.2\mu\text{s} + 0.5\mu\text{s})$



$V_A \rightarrow V_B$

$I_a > 0$



$V_A > V_B$

$V_B \rightarrow V_A$

- Voltage Edge Uncertainty effect


Matrix Converter linearization

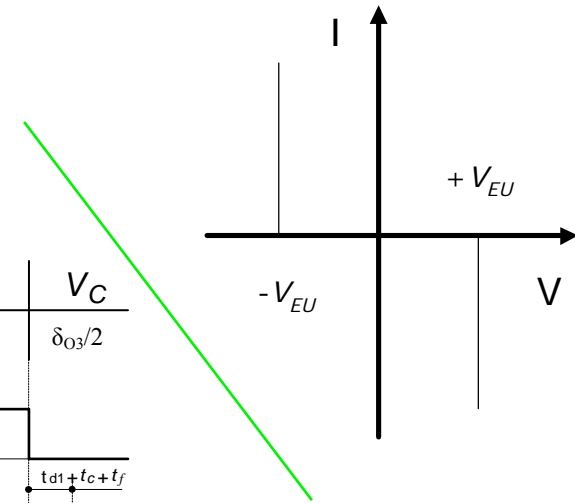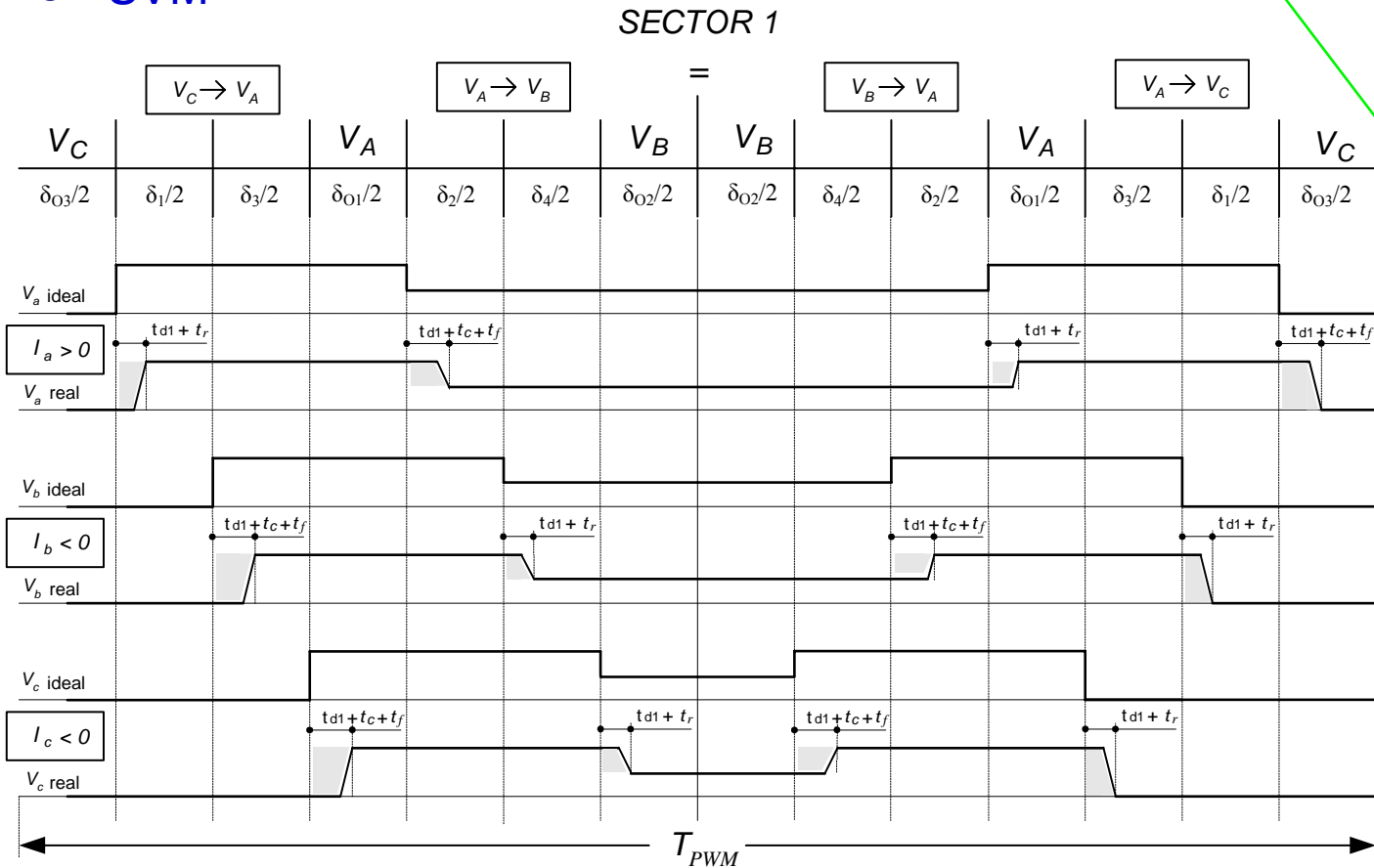- Model for Voltage Edge Uncertainty effect
- SVM





DUAL COMPENSATION


- Voltage Drop effect

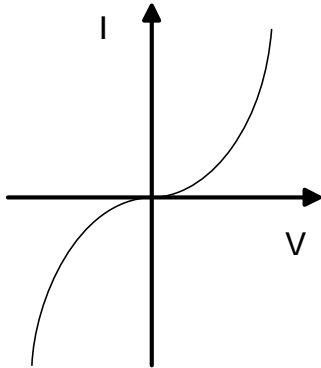






- Voltage Edge Uncertainty effect

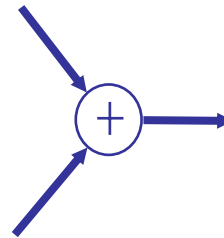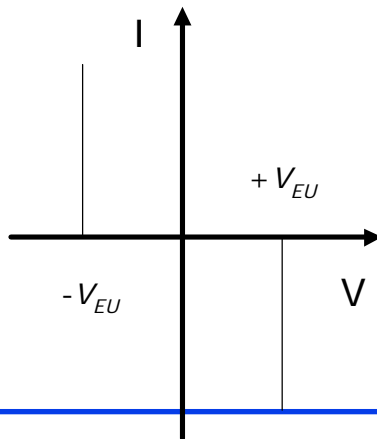

- Dual Compensation

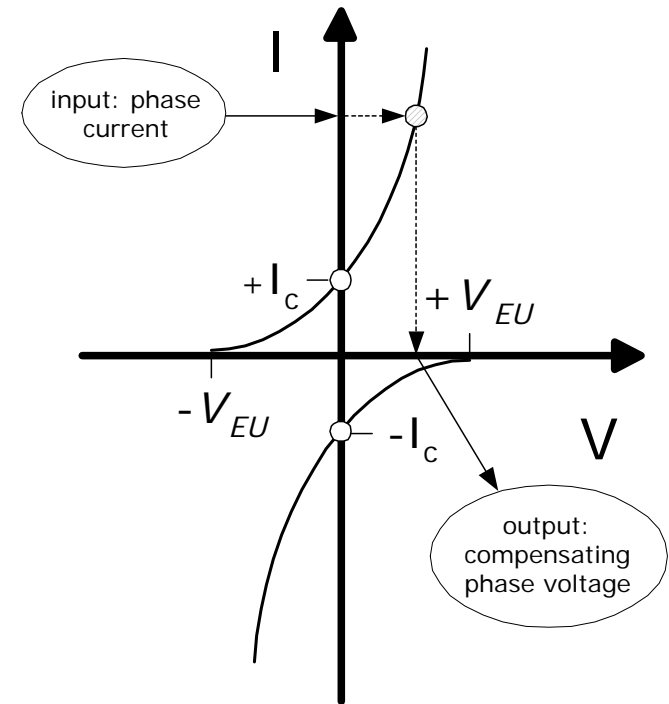

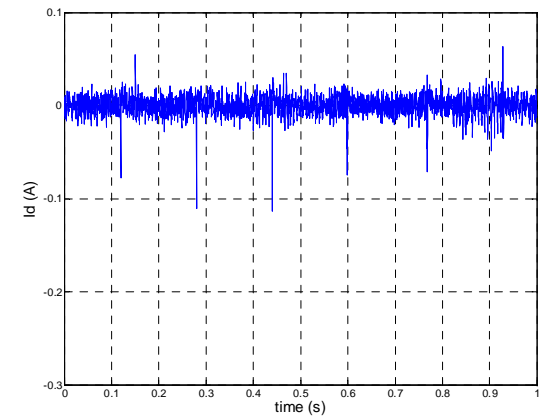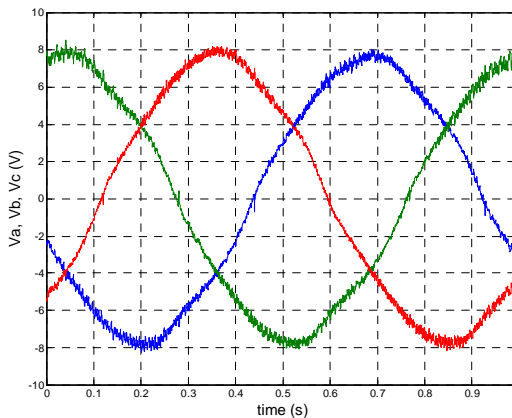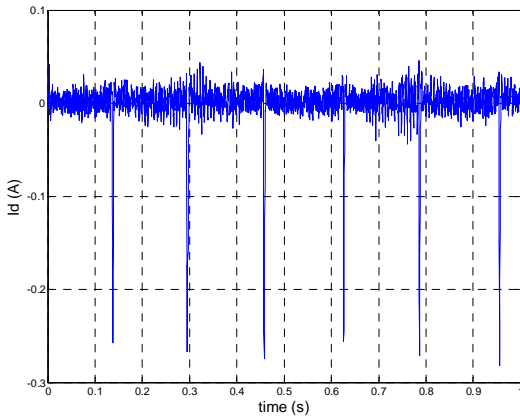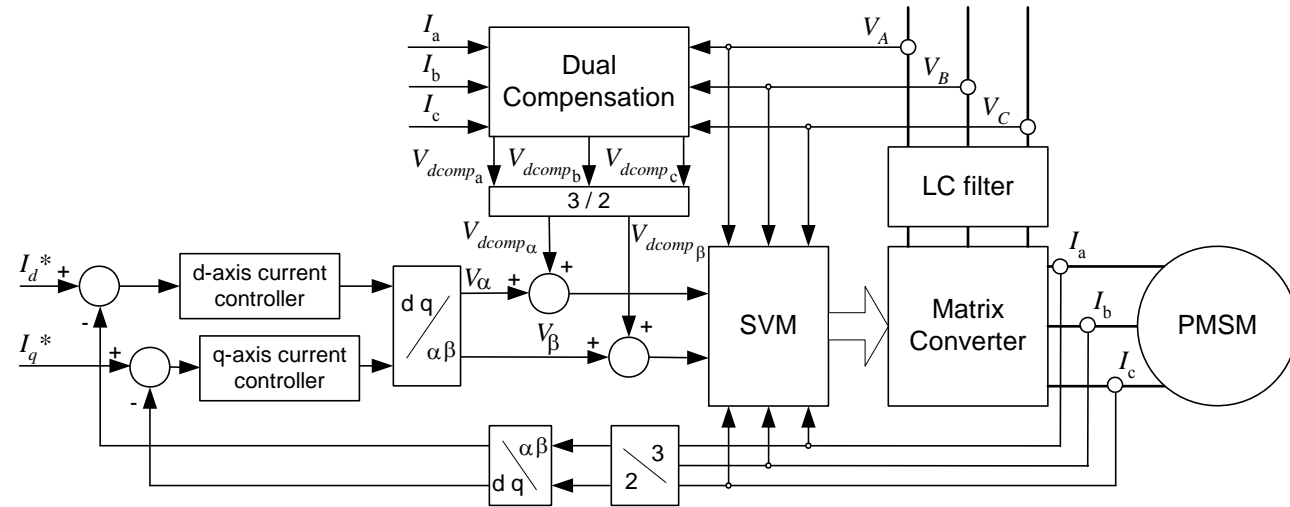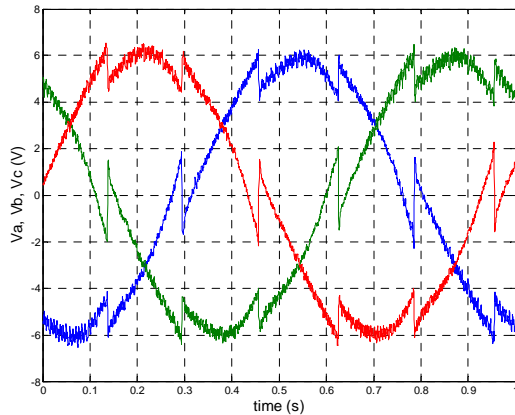Dual Compensation in Matrix Converters FOC Scheme_{Grid}



- Matrix Converter topology
 - 9 Bidirectional switch
- 4 step commutation
- Space Vector Modulation
- Input Filter
- Clamp Circuit
- Matrix Converter linearization
- Advantages of Matrix Converters:
 - Size
 - Sinusoidal input/output
 - Hostile environments
 - 4 quadrant

- *Applications*